No part of the candidate evidence in this exemplar material may be presented in an external assessment for the purpose of gaining credits towards an NCEA qualification.

91526





NEW ZEALAND QUALIFICATIONS AUTHORITY MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD KIA NOHO TAKATŪ KI TŌ ĀMUA AO!

Level 3 Physics, 2015

91526 Demonstrate understanding of electrical systems

9.30 a.m. Friday 20 November 2015 Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3–PHYSR.

In your answers use clear numerical working, words and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.


Check that this booklet has pages 2–8 in the correct order and that none of these pages is blank.

YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.




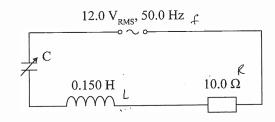QUESTION ONE: AC CIRCUITS


An AC circuit has a variable capacitor, an inductor, and a resistor in series, as shown below.



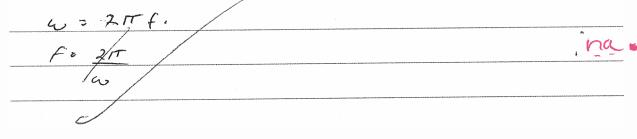(a) Calculate the angular frequency of the supply.



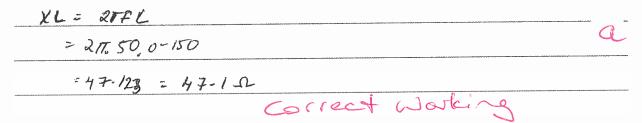(b) Show that the reactance of the inductor is 47.1Ω .



(c) When the variable capacitor has a value of 1.00×10^{-6} F, the voltage across the capacitor is measured as 20.9 V_{RMS} and the current flowing in the circuit is measured as 0.656 A_{RMS}.

Calculate the voltages across the inductor and the resistor, and draw labelled phasors showing the voltages across the capacitor, the inductor, and the resistor.

	(tr.
	NL NL
• •	()) on phasers
	Physics 91526, 2015

2

USE ONL

ASSESSOR'

(d) The variable capacitor is adjusted so that the circuit is now at resonance.

Explain, using physical principles, why the current is now a maximum, and calculate the value of the current in the circuit at resonance.


XI = Xc at resonance. 471 217F C V=IR. CE 47-1 2TF 47.1 0-44 37 = C = 0-15 corronadi. C 5 2550 = 0.44 A. Incar = V2 + mms. = VZ x 0.44 0.6277. 5 copact reacture of the capacitor and inductor are equal at resonance. The Current is now a maximum be cause as the voltage across the capacitor decreated due to the reactance of me capacitor. the anorrent was able to build up. hence ne acting maximum (Imax). . has identified that XL = Xc at - no idea that Z=R & is minimum : I is maximum. · incorrect calculation for I

QUESTION TWO: CAPACITORS

Dielectric constant of air = 1.00

Permittivity of free space = $8.85 \times 10^{-12} \text{ F m}^{-1}$

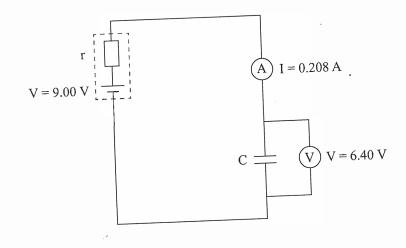A 9.00 V cell is being used to charge a capacitor, as shown below.




(a) At one point during the charging, the capacitor has a voltage of 6.40 V, and the current flowing in the circuit is 0.208 A.

Show that the internal resistance, r, of the cell is 12.5 Ω .

1=1R-	R = 6.40/0-208 = 30-76
$R = V_{\pm}$	9.00/0.208 = 43.26
1	1 20, 21: 12.5-1
Ryor =	43.76 30.28 12 3

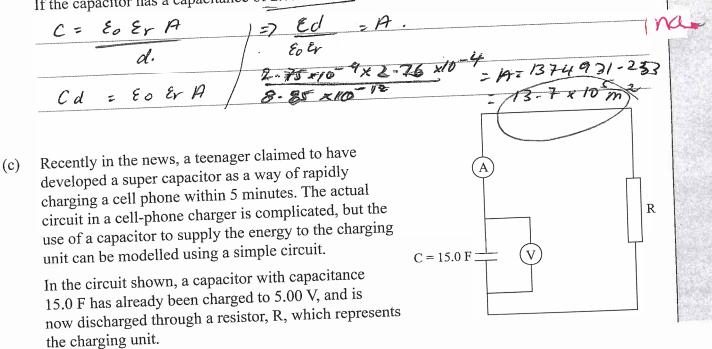
(b) The capacitor has air between its plates, and a plate separation of 2.26×10^{-4} m.

If the capacitor has a capacitance of 2.75×10^{-9} F, what is the overlap area of the plates?



4

ASSESSOR'S USE ONLY

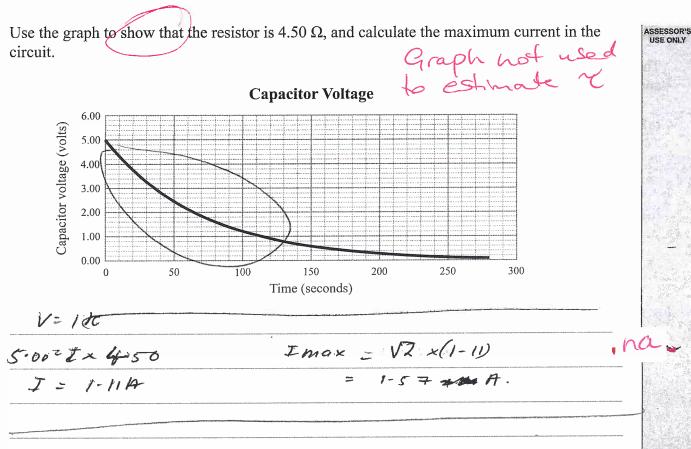

(d) One particular cell phone requires about 6×10^5 joules of energy to fully charge. A super capacitor of 400 F could be used to charge a cell phone that requires 5 V with a resistance of 4.5 Ω .

Use calculations to decide whether this capacitor would fully charge the cell phone within 5 minutes.

In your answer you should:

- calculate the time taken for the capacitor to become effectively discharged
- discuss whether the capacitor will release its energy within 5 minutes
- calculate the energy released by the capacitor when discharging through the resistor
- compare the energy released by the capacitor with the energy that would be required to fully charge a cell phone.

= 2000 J. Q = TERC 4.5 × 400 0 Correct = 1860 5. wente = 30 mins. For discharg 1/6 of ite mins it would only release in Thin 5 energy. tetal 6×16+5 x5 DE= 3000000 = 3.0×10'J. Physics 91526, 2015

5

USE ONLY


QUESTION THREE: ELECTROMAGNETIC INDUCTION

There are a number of techniques used to detect cars and bicycles waiting at traffic lights. The most common technique is the inductive loop circuit.

(a) State how an inductor stores energy.

by causing a buildup of voltage to the oppose to create incorsect answer charge.

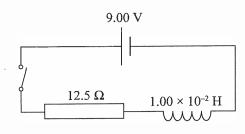(b) One type of inductor loop circuit is shown below. This circuit contains a 9.00 V battery, with an inductor of 1.00×10^{-2} H, and a total resistance of 12.5 Ω in the circuit.




Soon after closing the switch, the current is 0.260 A.

Find the voltage across the resistor and the voltage across the inductor, and therefore calculate the rate of change of current.

 $\frac{V = /R}{2} = 0.260 \times 12.5$ $\frac{V = 120}{2} = \frac{2.6 \times 10^{-3} V}{2}$ * na The rate of change of unrent has increased

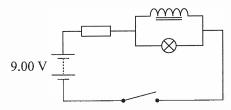(c) A different inductive loop circuit is constructed, as shown below.




When the switch is closed, the bulb is bright and then gets dimmer.

Explain, in terms of current, why the inductor makes the circuit behave this way.

according to Lenz low the charge must be opposed by an opposite change the voltage buildup is met by the magnetic thix causing all the voltage to go in the direction of the supply voltage (opposite direction).

Physics 91526, 2015

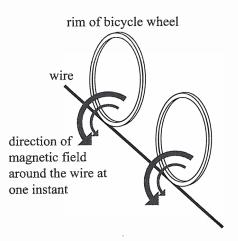(d) Inductive loops at traffic lights can be adjusted to detect bicycles with metal rims. Below is a simplified diagram of a bike waiting for the traffic lights to change.



The inductive loop circuit uses Faraday's law to detect changes in the inductance when a bicycle is above the circuit. The high-frequency, alternating current induces a magnetic field in the metal bicycle rim. The magnetic field induced in the bicycle rim reduces the overall magnetic field. The inductance of the circuit is reduced, and this is detected by the traffic lights.

Explain the underlying physical concepts used in this situation.

In your answer you should:

- describe the nature of the magnetic field that is created by the alternating current in the wire
- explain why a high-frequency alternating current is needed to induce a significant magnetic field in the rims of the bicycle wheels
- explain why the induced magnetic field in the rims of the bicycle wheels is in the opposite direction to the magnetic field around the wire.

the magnetic sield moves from north to south. 17 small because the rim of the bicycle wheel (less surface anea) more range (otronger magneticfield, to be detated the bigeves 13 needed for opposing (force bicycle The maquesic field de ha detected IF to be 54 direction the nay netd Samo amplified. The traffic schall be distribunce in nagnetic to the presence biggele. them Physics 91526, 2015 notice of no understa

7

ASSESSOR'