

3

91526



NEW ZEALAND QUALIFICATIONS AUTHORITY
MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD
KIA NOHO TAKATŪ KI TŌ ĀMUA AO!

SUPERVISOR'S USE ONLY

Level 3 Physics, 2015

91526 Demonstrate understanding of electrical systems

9.30 a.m. Friday 20 November 2015
Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3-PHYSR.

In your answers use clear numerical working, words and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–8 in the correct order and that none of these pages is blank.


YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.

TOTAL

ASSESSOR'S USE ONLY

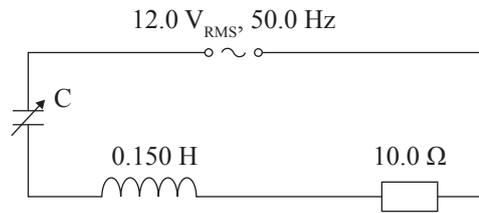QUESTION ONE: AC CIRCUITS

An AC circuit has a variable capacitor, an inductor, and a resistor in series, as shown below.




- (a) Calculate the angular frequency of the supply.

- (b) Show that the reactance of the inductor is 47.1Ω .

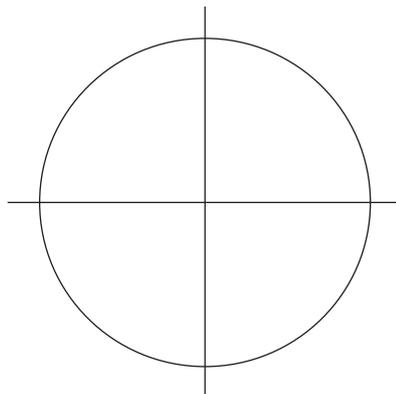- (c) When the variable capacitor has a value of $1.00 \times 10^{-6} \text{ F}$, the voltage across the capacitor is measured as $20.9 \text{ V}_{\text{RMS}}$ and the current flowing in the circuit is measured as $0.656 \text{ A}_{\text{RMS}}$.

Calculate the voltages across the inductor and the resistor, and draw labelled phasors showing the voltages across the capacitor, the inductor, and the resistor.




QUESTION TWO: CAPACITORS

Dielectric constant of air = 1.00

Permittivity of free space = $8.85 \times 10^{-12} \text{ F m}^{-1}$

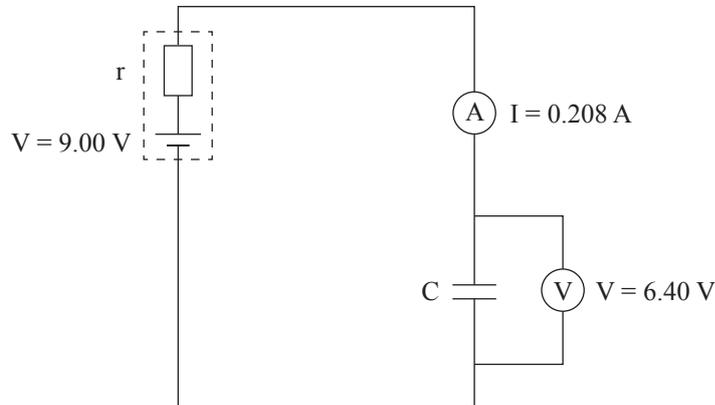A 9.00 V cell is being used to charge a capacitor, as shown below.



- (a) At one point during the charging, the capacitor has a voltage of 6.40 V, and the current flowing in the circuit is 0.208 A.


Show that the internal resistance, r , of the cell is 12.5Ω .

- (b) The capacitor has air between its plates, and a plate separation of $2.26 \times 10^{-4} \text{ m}$.

If the capacitor has a capacitance of $2.75 \times 10^{-9} \text{ F}$, what is the overlap area of the plates?

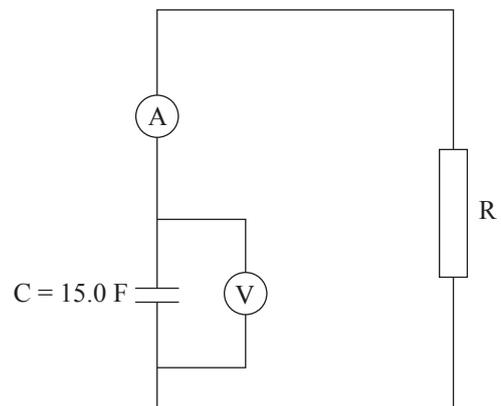
- (c) Recently in the news, a teenager claimed to have developed a super capacitor as a way of rapidly charging a cell phone within 5 minutes. The actual circuit in a cell-phone charger is complicated, but the use of a capacitor to supply the energy to the charging unit can be modelled using a simple circuit.

In the circuit shown, a capacitor with capacitance 15.0 F has already been charged to 5.00 V , and is now discharged through a resistor, R , which represents the charging unit.



Use the graph to show that the resistor is 4.50Ω , and calculate the maximum current in the circuit.

ASSESSOR'S
USE ONLY

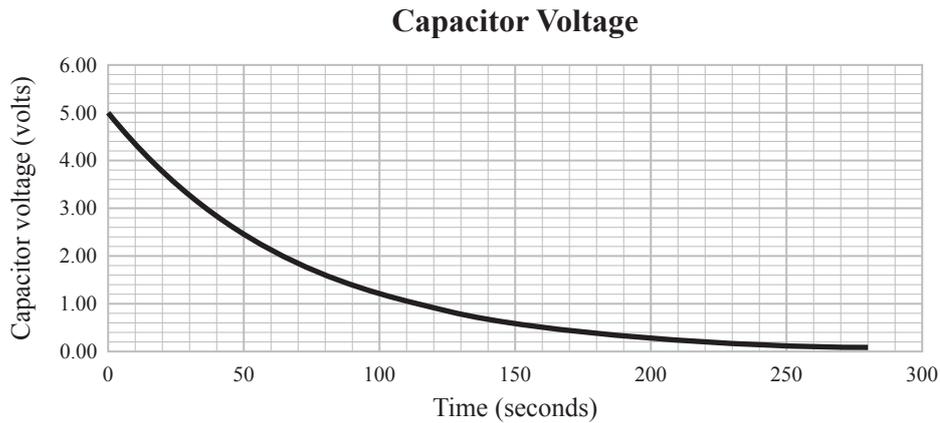

- (d) One particular cell phone requires about 6×10^5 joules of energy to fully charge. A super capacitor of 400 F could be used to charge a cell phone that requires 5 V with a resistance of 4.5Ω .

Use calculations to decide whether this capacitor would fully charge the cell phone within 5 minutes.

In your answer you should:


- calculate the time taken for the capacitor to become effectively discharged
- discuss whether the capacitor will release its energy within 5 minutes
- calculate the energy released by the capacitor when discharging through the resistor
- compare the energy released by the capacitor with the energy that would be required to fully charge a cell phone.

QUESTION THREE: ELECTROMAGNETIC INDUCTION

There are a number of techniques used to detect cars and bicycles waiting at traffic lights. The most common technique is the inductive loop circuit.

- (a) State how an inductor stores energy.

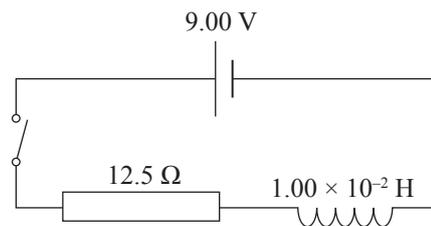
- (b) One type of inductor loop circuit is shown below. This circuit contains a 9.00 V battery, with an inductor of 1.00×10^{-2} H, and a total resistance of 12.5Ω in the circuit.



Soon after closing the switch, the current is 0.260 A.

Find the voltage across the resistor and the voltage across the inductor, and therefore calculate the rate of change of current.

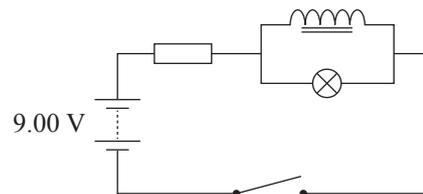- (c) A different inductive loop circuit is constructed, as shown below.



When the switch is closed, the bulb is bright and then gets dimmer.

Explain, in terms of current, why the inductor makes the circuit behave this way.
