

No part of the candidate evidence in this exemplar material may be presented in an external assessment for the purpose of gaining credits towards an NCEA qualification.

3

91526



NEW ZEALAND QUALIFICATIONS AUTHORITY  
MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD  
KIA NOHO TAKATŪ KI TŌ ĀMUA AO!

SUPERVISOR'S USE ONLY

## Level 3 Physics, 2015

### 91526 Demonstrate understanding of electrical systems

9.30 a.m. Friday 20 November 2015  
Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

**You should attempt ALL the questions in this booklet.**

Make sure that you have Resource Booklet L3-PHYSR.

In your answers use clear numerical working, words and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–8 in the correct order and that none of these pages is blank.

**YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.**

**Merit**

**TOTAL**


**17**

ASSESSOR'S USE ONLY
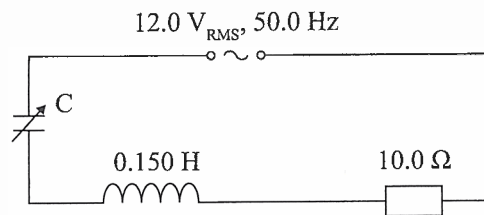
# QUESTION ONE: AC CIRCUITS

ASSESSOR'S  
USE ONLY

An AC circuit has a variable capacitor, an inductor, and a resistor in series, as shown below.



- (a) Calculate the angular frequency of the supply.

$$\begin{aligned}\omega &= 2\pi f \\ &= 2 \times 3.14 \times 50.0 \\ &= \underline{314 \text{ rad s}^{-1} \text{ Hz}}\end{aligned}$$

- (b) Show that the reactance of the inductor is  $47.1 \Omega$ .


$$\begin{aligned}X_L &= 2\pi fL \\ &= 2 \times 3.14 \times 50 \times 0.150 \\ &= \underline{47.1 \Omega}\end{aligned}$$

- (c) When the variable capacitor has a value of  $1.00 \times 10^{-6} \text{ F}$ , the voltage across the capacitor is measured as  $20.9 \text{ V}_{\text{RMS}}$  and the current flowing in the circuit is measured as  $0.656 \text{ A}_{\text{RMS}}$ .

Calculate the voltages across the inductor and the resistor, and draw labelled phasors showing the voltages across the capacitor, the inductor, and the resistor.

$$\begin{aligned}V_{\text{resistor}} &= I \times R \\ V_{\text{inductor}} &= I \times X_L \\ &= 0.656 \times 10 \\ &= \underline{6.56 \text{ V}} \\ &= 47.1 \times 0.656 = \underline{30.9 \text{ V}}\end{aligned}$$

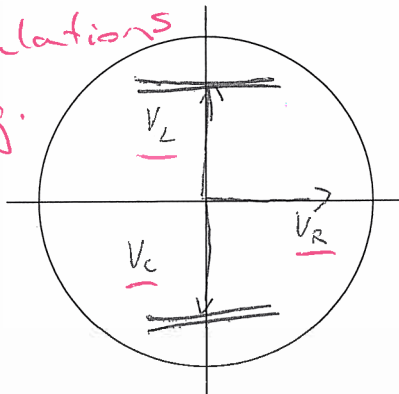Correct calculations  
& phasor diag.  
but sizes  
incorrect.



- (d) The variable capacitor is adjusted so that the circuit is now at resonance.

Explain, using physical principles, why the current is now a maximum, and calculate the value of the current in the circuit at resonance.

At resonance,  $X_L = X_C$  and they cancel each other out. Hence the impedance of circuit is only gotten from the resistor and it is at minimum. Because the impedance is minimum current flows at maximum.

$$\begin{aligned}
 I_{\text{resonance}} &= \frac{V}{Z} \\
 &= \frac{12}{10} \\
 &= 1.2 \text{ A}
 \end{aligned}$$

Understanding that current is max because  $Z$  is minimum due to  $X_L$  &  $X_C$  cancelled out.

2


E7

## QUESTION TWO: CAPACITORS

Dielectric constant of air = 1.00

Permittivity of free space =  $8.85 \times 10^{-12} \text{ F m}^{-1}$

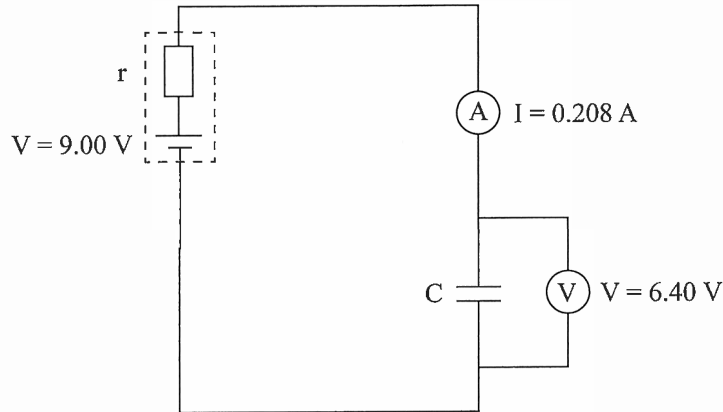A 9.00 V cell is being used to charge a capacitor, as shown below.



$$V = \mathcal{E} - Ir$$

$$6.4 = 9 - 0.208r$$

- (a) At one point during the charging, the capacitor has a voltage of 6.40 V, and the current flowing in the circuit is 0.208 A.

Show that the internal resistance,  $r$ , of the cell is  $12.5 \Omega$ .

$$V = \mathcal{E} - Ir$$

$$6.4 = 9 - 0.208r$$

$$r = 12.5 \Omega$$

- (b) The capacitor has air between its plates, and a plate separation of  $2.26 \times 10^{-4} \text{ m}$ .

If the capacitor has a capacitance of  $2.75 \times 10^{-9} \text{ F}$ , what is the overlap area of the plates?


$$C = \frac{\epsilon_0 A}{d}$$

$$2.75 \times 10^{-9} = \frac{8.85 \times 10^{-12} A}{2.26 \times 10^{-4}}$$

$$A = 0.0702 \text{ m}^2$$

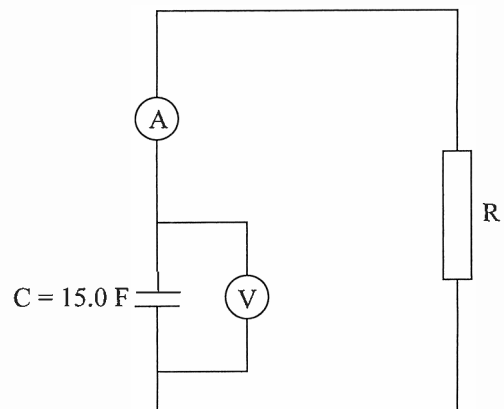
- (c) Recently in the news, a teenager claimed to have developed a super capacitor as a way of rapidly charging a cell phone within 5 minutes. The actual circuit in a cell-phone charger is complicated, but the use of a capacitor to supply the energy to the charging unit can be modelled using a simple circuit.

In the circuit shown, a capacitor with capacitance 15.0 F has already been charged to 5.00 V, and is now discharged through a resistor,  $R$ , which represents the charging unit.



Use the graph to show that the resistor is  $4.50\ \Omega$ , and calculate the maximum current in the circuit.

ASSESSOR'S  
USE ONLY

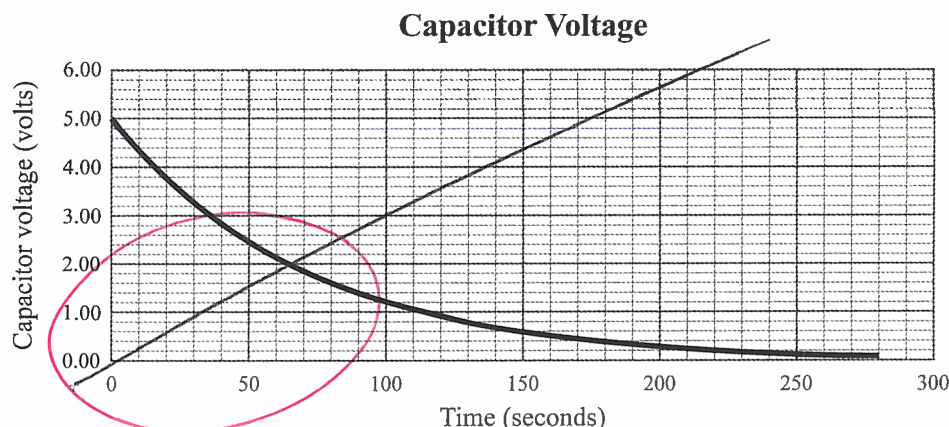

$$V = IR$$

the time constant voltage =  $37\% \times 5.00$        $R = \frac{68}{15}$   
 $= 1.85V$        $= 4.50\ \Omega$

$$\tau = 68s$$

$$I = \frac{5}{4.50}$$

$$\tau = RC$$

$$> 1.1A$$

- (d) One particular cell phone requires about  $6 \times 10^5$  joules of energy to fully charge. A super capacitor of  $400\ F$  could be used to charge a cell phone that requires  $5\ V$  with a resistance of  $4.5\ \Omega$ .

Use calculations to decide whether this capacitor would fully charge the cell phone within 5 minutes.

In your answer you should:

- calculate the time taken for the capacitor to become effectively discharged
- discuss whether the capacitor will release its energy within 5 minutes
- calculate the energy released by the capacitor when discharging through the resistor
- compare the energy released by the capacitor with the energy that would be required to fully charge a cell phone.

Time taken for discharge = ~~270s~~ Has not calculated

$$E = \frac{1}{2} CV^2$$

$$= \frac{1}{2} \times 400 \times 5^2$$

$$= 5000J$$

the time taken to fully discharge correctly, this is also required for 'e'

The capacitor will release its energy within 5 minutes

because it only takes  $270s$  ( $4.5\ min$ ) for it to fully discharge. The energy released by capacitor will not be able to fully charge a cell phone, as it is too small.



### QUESTION THREE: ELECTROMAGNETIC INDUCTION


ASSESSOR'S  
USE ONLY

There are a number of techniques used to detect cars and bicycles waiting at traffic lights. The most common technique is the inductive loop circuit.

- (a) State how an inductor stores energy.

The steady current causes a magnetic field throughout the coil where energy can be stored.

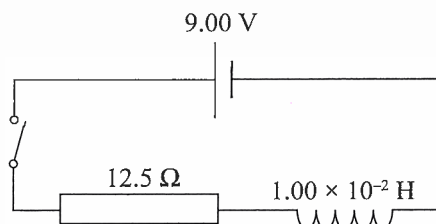- (b) One type of inductor loop circuit is shown below. This circuit contains a 9.00 V battery, with an inductor of  $1.00 \times 10^{-2} \text{ H}$ , and a total resistance of  $12.5 \Omega$  in the circuit.



Soon after closing the switch, the current is 0.260 A.

Find the voltage across the resistor and the voltage across the inductor, and therefore calculate the rate of change of current.

$V = IR$

$$V_{\text{resistor}} = 0.260 \times 12.5 = 2.575 \text{ V}$$

$$V_{\text{inductor}} = 9.00 - 2.575 = 6.425 \text{ V}$$


$$\epsilon = -L \frac{\Delta I}{\Delta t}$$

$$6.425 = -1.00 \times 10^{-2} \frac{\Delta I}{\Delta t}$$

$$\frac{\Delta I}{\Delta t} = 643 \text{ A s}^{-1}$$

minor calculation error

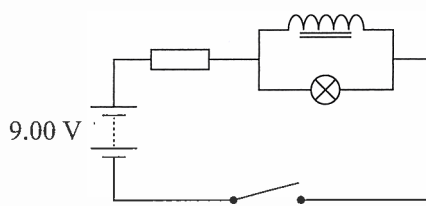- (c) A different inductive loop circuit is constructed, as shown below.



Correct idea that inductor produces induced voltage due to  $\Delta \Phi$

When the switch is closed, the bulb is bright and then gets dimmer.

Explain, in terms of current, why the inductor makes the circuit behave this way.

When current flow into conductor this causes a change in magnetic flux creating an induced voltage (Faraday's Law). An induced current is produced which opposes the incoming current (Lenz's Law). This prevents current from flowing to the bulb and hence it gets dimmer.

- 
- rim of bicycle wheel
- wire
- direction of magnetic field around the wire at one instant

- describe the nature of the magnetic field that is created by the alternating current in the wire
- explain why a high-frequency alternating current is needed to induce a significant magnetic field in the rims of the bicycle wheels
- explain why the induced magnetic field in the rims of the bicycle wheels is in the opposite direction to the magnetic field around the wire.

This image shows a single sheet of white paper with horizontal blue or grey ruling lines. The lines are evenly spaced and run across the width of the page. On the left side, there is a vertical crease or fold line, suggesting the paper might be part of a notebook or binder. The paper appears slightly aged or off-white. There is no handwriting or other markings on the page.