

# 3

91526M



NEW ZEALAND QUALIFICATIONS AUTHORITY  
MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD  
KIA NOHO TAKATŪ KI TŌ ĀMUA AO!

SUPERVISOR'S USE ONLY

## Ahupūngao, Kaupae 3, 2016

### 91526M Te whakaatu māramatanga ki ngā pūnaha hiko

2.00 i te ahiahi Rātū 15 Whiringa-ā-rangi 2016  
Whiwhinga: Ono

Paetae	Kaiaka	Kairangi
Te whakaatu māramatanga ki ngā pūnaha hiko.	Te whakaatu māramatanga hōhonu ki ngā pūnaha hiko.	Te whakaatu māramatanga matawhānui ki ngā pūnaha hiko.

Tirohia mēnā e rite ana te Tau Ākonga ā-Motu (NSN) kei runga i tō puka whakauru ki te tau kei runga i tēnei whārangi.

#### Me whakamātau koe i ngā tūmahi KATOA kei roto i tēnei pukapuka.

Tirohia mēnā kei a koe te Pukapuka Rauemi L3-PHYSMR.

Ki roto i ō tuhinga, whakamahia ngā whiriwhiringa tohutu mārama, ngā kupu, ngā hoahoa hoki, tētahi, ētahi rānei o ēnei, ki hea hiahiatia ai.

Me hoatu te wae tika o te Pūnaha Waeine ā-Ao (SI) ki ngā tuhinga tohutu, ki ngā tau tika o ngā tau tāpua.

Mēnā ka hiahia whārangi atu anō mō ō tuhinga, whakamahia te wāhi wātea kei muri o tēnei pukapuka.

Tirohia mēnā e tika ana te raupapatanga o ngā whārangi 2–15 kei roto i tēnei pukapuka, ka mutu, kāore tētahi o aua whārangi i te takoto kau.

#### ME HOATU RAWA KOE I TĒNEI PUKAPUKA KI TE KAIWHAKAHAERE Ā TE MUTUNGA O TE WHAKAMĀTAUTAU.


TAPEKE

MĀ TE KAIMĀKA ANAKE
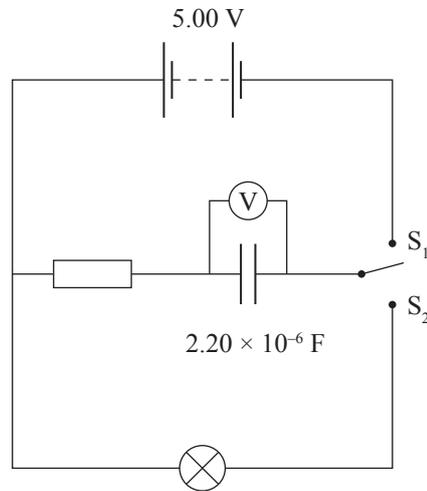
## TŪMAHI TUATAHI: TE WHAKAHIKO PŪNGA IAHIKO

Ka whakatūhia e Eleanor he ara iahiko hei tūhura he pēhea te mahi a ngā pūnga iahiko. Ko te ara iahiko e whakaaturia ana i raro nei.

Kei roto i te ara iahiko ko tētahi pūnga iahiko  $2.20 \times 10^{-6}$  F me tētahi pana pito rua.




- (a) Tātaihia te whana mōrahi e putua ana e te pūnga iahiko i roto i tēnei ara iahiko.

---



---

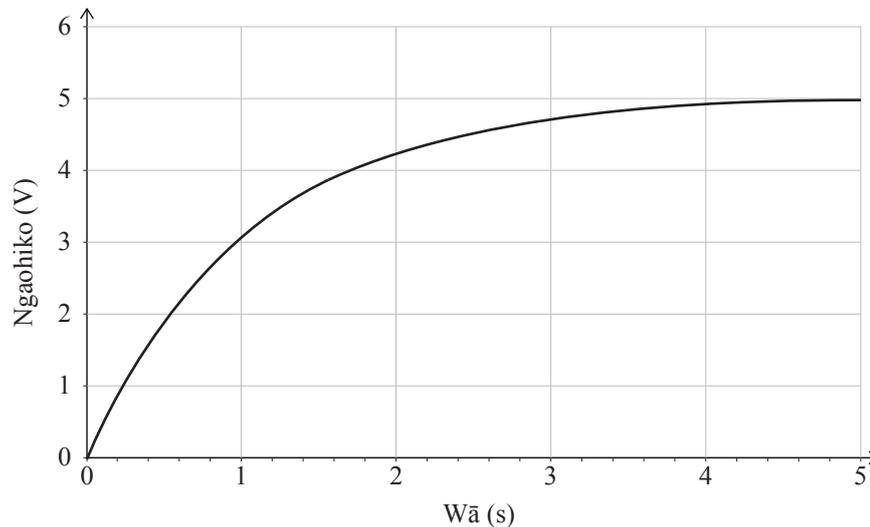Kei te hiko-kore te pūnga iahiko i te tuatahi, ā, e whakaaturia ana te tūnga o te pana. Ka nekehia e Eleanor te pana ki S<sub>1</sub>, ā, ka whakahiko haere te pūnga iahiko. E whakaaturia ana i raro te kauwhata o te ngaohiko pūnga iahiko ki te wā.



- (b) Mai i te kauwhata, tātaihia te parenga o te parenga iahiko.

Tātuhia ngā rārangi ki te kauwhata hei āwhina ki te whakamārama i ō mahinga.

---




---



---

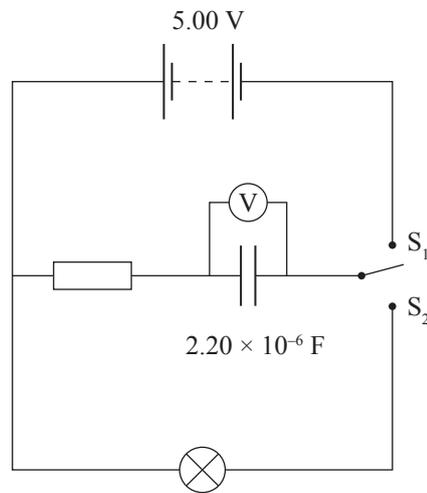**QUESTION ONE: CHARGING A CAPACITOR**

Eleanor sets up a circuit to investigate how capacitors operate. The circuit is shown below. The circuit includes a  $2.20 \times 10^{-6}$  F capacitor and a double pole switch.




- (a) Calculate the maximum charge stored by the capacitor in this circuit.

---



---

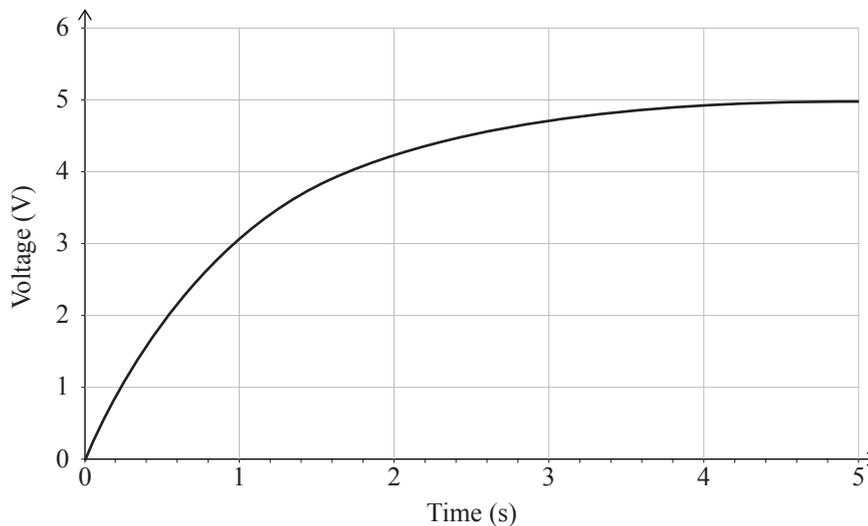The capacitor is initially uncharged, and the switch is in the position shown. Eleanor moves the switch to  $S_1$  and the capacitor charges up. A graph of the capacitor voltage against time is shown below.



- (b) Use the graph to calculate the resistance of the resistor.  
Draw lines on the graph to help explain your working.

---



---



---





## TŪMAHI TUARUA: TE WHITIHIKO

Whakamahia ai ngā whitihiko hei whakapiki, whakaheke rānei i te rahinga o tētahi ngaohiko AC. He whitihiko tā Wei i hangaia hei whakawhiti i te 240 V ki te 12.0 V.

E 40 ngā hurihanga o te pōkai tuarua.

- (a) Tātaihia te maha o ngā huringa o te pōkai matua.

---



---



---

- (b) Whakamāramahia mai he pēhea te hanga a tētahi ngaohiko hohoko puta noa i te pōkai matua i tētahi iahiko hohoko i roto i tētahi pūrāma e tūhonoa ana ki te pōkai tuarua.

---



---



---



---



---




---



---

Ka mahi ia pōkai o tētahi whitihiko hei pūkōpana (inductor).

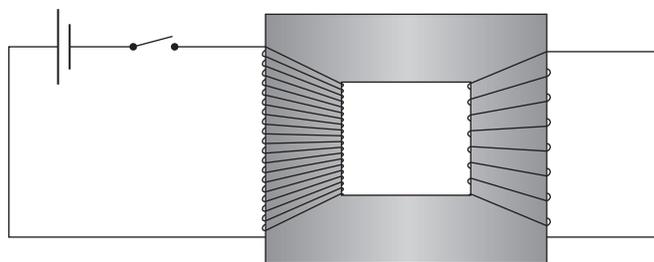Kei te mau tētahi pōkai matua ki tētahi pūhiko, pana hoki e ai ki te hoahoa i raro. Kei te kati te pana, ā, i muri mai ka huakina.



**QUESTION TWO: THE TRANSFORMER**

Transformers can be used to increase or decrease the size of an AC voltage. Wei has a transformer that is designed to convert 240 V into 12.0 V.

The secondary coil has 40 turns.

- (a) Calculate the number of turns on the primary coil.

---

---

---

- (b) Explain how an alternating voltage across the primary coil creates an alternating current in a light bulb connected to the secondary coil.

---

---

---

---

---


---

---

---

Each coil of a transformer acts as an inductor.

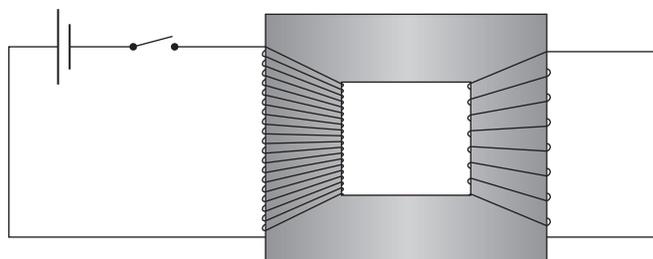A primary coil is attached to a battery and switch as shown in the diagram below. The switch is closed and then some time later the switch is opened.







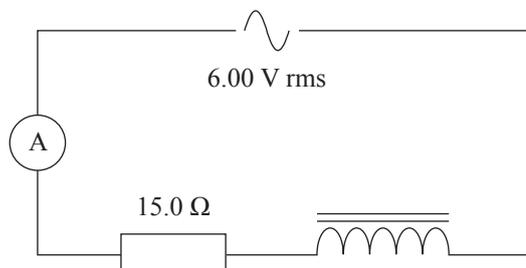
## TŪMAHI TUATORU: TE INE RINO I ROTO KIRIKIRI

Kei te hiahia a Vivienne ki te ine i te nui o te rino i roto i ngā ranunga kirikiri-rino mai i ngā ākau rerekē. E whakaatu ana te hoahoa i raro i te ara iahiko e whakamahi ana ia. Kei roto i te ara iahiko tētahi pūkai huri-500 me te parenga o te  $15.0 \Omega$ , me tētahi putunga AC.

Ka mahi te pūkai pēnei i tētahi parenga iahiko me tētahi pūkōpana e hātepetia ana.



He uho arenga tō te pūkai, kāore he mea i roto i te tuatahi. Ka whakatikatika a Vivienne i te ngaohiko punahiko ki te 6.00 V rms.

- (a) Tātaitia te mōrahi ngaohiko inamata puta noa i te punahiko.

---



---

I te wā whakamātautau, ka raua e Vivienne he ranunga rino me te kirikiri ki roto i te uho o te pūkai.

- (b) Tuhia he aha te pānga o tēnei ki te rahi o te hohenga o te pūkai.

Mā te kōrero mō te haukotinga (impedance), whakamāramahia mai ka ahatia te rahinga o te iahiko i roto i te ara iahiko i a ia e tāpiri ana i te ranunga rino me te kirikiri.

---



---



---




---

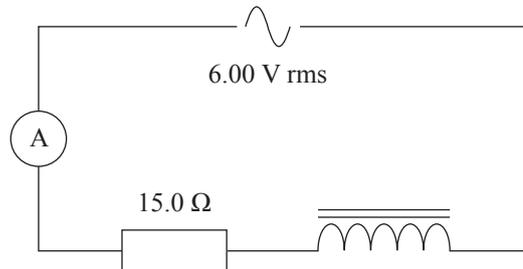**QUESTION THREE: MEASURING IRON IN SAND**

Vivienne wants to measure the amount of iron in iron-sand mixtures collected from different beaches. The diagram below shows the circuit that she uses. The circuit includes a 500-turn coil with a resistance of  $15.0\ \Omega$ , and an AC supply.

The coil behaves like a resistor and an inductor in series.



The coil has a hollow core that is initially empty. Vivienne adjusts the power supply voltage to 6.00 V rms.

- (a) Calculate the instantaneous maximum (peak) voltage across the power supply.

---



---

During testing, Vivienne puts a mixture of iron and sand inside the core of the coil.

- (b) State what effect this has on the size of the coil's reactance.

With reference to impedance, explain what happens to the size of the current in the circuit as she adds the mixture of iron and sand.

---



---



---



---









*English translation of the wording on the front cover*

## Level 3 Physics, 2016

### 91526 Demonstrate understanding of electrical systems

2.00 p.m. Tuesday 15 November 2016  
Credits: Six

91526M

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

**You should attempt ALL the questions in this booklet.**

Make sure that you have Resource Booklet L3–PHYSMR.

In your answers use clear numerical working, words and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–15 in the correct order and that none of these pages is blank.

**YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.**