

3

91526



NEW ZEALAND QUALIFICATIONS AUTHORITY
MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD
KIA NOHO TAKATŪ KI TŌ ĀMUA AO!

SUPERVISOR'S USE ONLY

Tick this box if you
have NOT written
in this booklet

Level 3 Physics 2022

91526 Demonstrate understanding of electrical systems

Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3–PHYSR.

In your answers use clear numerical working, words, and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.


Check that this booklet has pages 2–8 in the correct order and that none of these pages is blank.

Do not write in any cross-hatched area (). This area may be cut off when the booklet is marked.

YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.

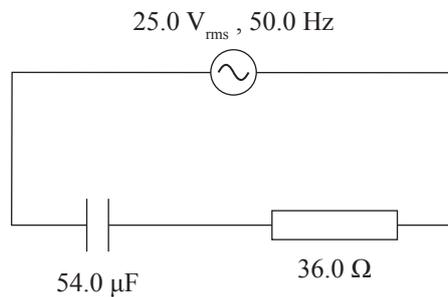QUESTION ONE: AC CIRCUITS

George is investigating AC circuits. He connects a $54.0 \mu\text{F}$ ($54.0 \times 10^{-6} \text{ F}$) capacitor in series with a 36.0Ω resistor and a $25.0 \text{ V}_{\text{rms}}$, 50.0 Hz AC supply, as shown in the diagram below.




- (a) Show that the reactance of the capacitor is 58.9Ω .

- (b) Calculate the circuit current.

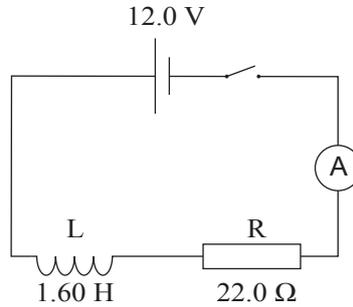QUESTION TWO: ELECTROMAGNETISM

David is investigating inductors and magnets.

He uses a 1.60 H , 22.0Ω inductor, and connects it to a 12.0 V power supply. The inductor can be considered as a pure inductor in series with a resistor, as shown in the diagram below.



- (a) Calculate the circuit current **after two time constants**, once the switch is closed and current begins to flow.

- (b) State the voltage across the pure inductor and the voltage across the resistor once the current is steady.

Voltage across the pure inductor = _____

Voltage across the resistor = _____


- (c) Once the current has reached a steady value, the switch is opened, and current falls to zero in $2.50 \times 10^{-2} \text{ s}$.

Calculate the size of the average induced voltage.

State the direction of the induced voltage across the inductor.

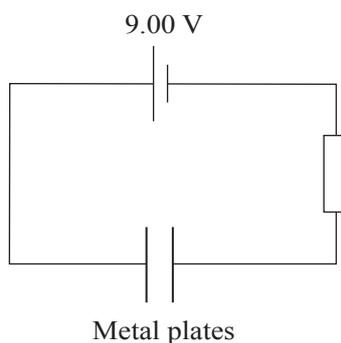QUESTION THREE: CAPACITORS IN DC CIRCUITS

Anne is carrying out some experiments using parallel metal plates to investigate capacitors. She takes a pair of metal plates with an area of 0.160 m^2 and connects them to a 9.00 V DC supply.



The plates of the air-filled capacitor ($\epsilon_{\text{air}} = 1.00$), are separated by a distance of $1.00 \times 10^{-3} \text{ m}$.

- (a) Show that the capacitance of the capacitor is $1.42 \times 10^{-9} \text{ F}$.

- (b) (i) Calculate the energy stored in the capacitor once it is fully charged.


- (ii) Describe the effect on the energy stored in the capacitor when a sheet of mica with relative permittivity of 7.00 is introduced between the capacitor plates.

- (c) Anne then disconnects the plates from the 9.00 V DC supply, so that the plates are electrically isolated. She then pulls the plates apart.

Explain what would happen to:

- the charge on the plates
- the voltage across the plates.

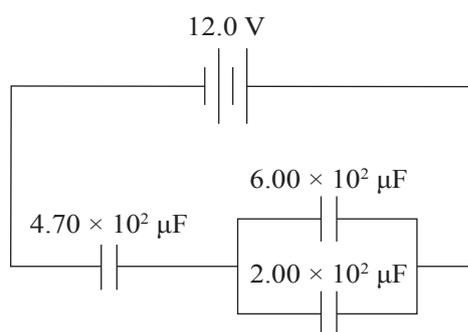- (d) Anne then experiments with connecting some different capacitors, in series and in parallel, across a 12.0 V supply, as shown in the diagram below.



Calculate the voltage across the $4.70 \times 10^2 \mu\text{F}$ capacitor.

Begin your answer by calculating the total capacitance.
