



SUPERVISOR'S USE ONLY

3Draw a cross through the box (☒)
if you have NOT written in this booklet

+

91526

915260

**Mana Tohu Mātauranga o Aotearoa**
New Zealand Qualifications Authority

Level 3 Physics 2023

91526 Demonstrate understanding of electrical systems

Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3-PHYSR.

In your answers use clear numerical working, words, and/or diagrams as required.

Numerical answers should be given with an appropriate SI unit.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–12 in the correct order and that none of these pages is blank.

Do not write in any cross-hatched area (DO NOT WRITE). This area will be cut off when the booklet is marked.

YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.


QUESTION ONE: CAPACITORS

Kate is learning about capacitors. She investigates a capacitor found in a camera. The capacitor is labelled 185 nF ($1.85 \times 10^{-7} \text{ F}$).

- (a) The camera also contains a 1.50 V (“AA”) battery.

Show that the energy stored by the capacitor, when it is fully charged by connecting it to the battery, is $2.08 \times 10^{-7} \text{ J}$.

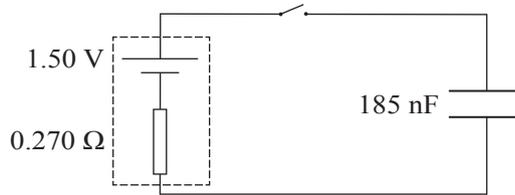- (b) The diagram below shows the circuit used to charge the capacitor. The battery has an internal resistance of 0.270Ω . Assume the rest of the circuit has no resistance.




Sketch a curve by plotting at least four points on the grid opposite to show how the charge on the capacitor plates varies with time, once the switch is closed.

Your answer should indicate:

- the time constant for charging the capacitor
- the maximum charge that will be stored on the capacitor plates.

Show all calculations clearly.

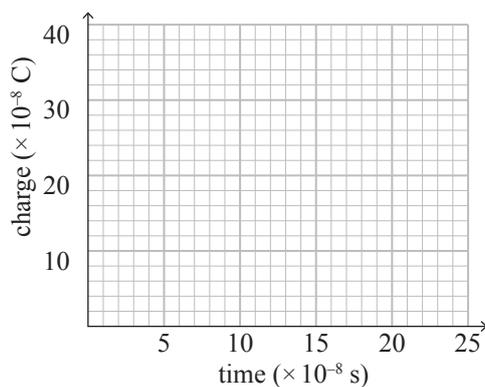

If you
need to
redraw your
response, use
the grid on
page 10.

- (c) Although the capacitor plates are rolled up, they act like two metal rectangles measuring $3.2 \times 10^{-2} \text{ m} \times 1.83 \text{ m}$, with dielectric material in between.

If the dielectric material in the capacitor has a relative permittivity of 2.10, calculate the distance between the metal rectangles.


**This page has been deliberately left blank.
The assessment continues on the following page.**

QUESTION TWO : TRANSFORMERS AND INDUCTORS

Kate's school has a demonstration transformer, pictured alongside. She connects the 12 000-turn primary coil (red in the picture) to the mains supply (240 V rms).

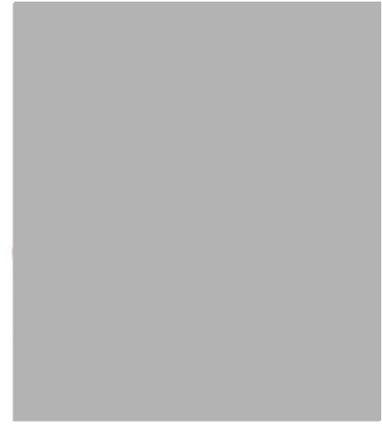- (a) She connects an AC voltmeter to the blue coil.

Calculate the rms voltage she would measure from the 600-turn secondary coil.



Source: www.findel-international.com/product/science/physics/electricity-and-electromagnetism/dissectible-transformer/e8h26564

- (b) The two coils are held by a ring of laminated soft iron, which runs through the core of each coil.

Explain why:

- an AC voltage in the red coil produces an AC voltage in the blue (secondary) coil
- the coils are wrapped around an iron ring.

SPARE DIAGRAM

If you need to redraw your response to Question One (b), use the grid below. Make sure it is clear which answer you want marked.

