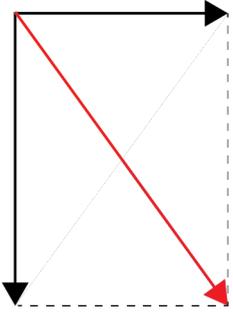


Assessment Schedule – 2022**Physics: Demonstrate understanding of electrical systems (91526)****Evidence**

Q	Evidence	Achievement	Merit	Excellence
ONE (a)	$X_c = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 54.0 \times 10^{-6}}$ $= 58.946 \Omega$	<ul style="list-style-type: none"> • Correct formula and substitution. 		
(b)	$Z = \sqrt{R^2 + X_c^2}$ $= \sqrt{36.0^2 + 58.9^2} = 69.1 \Omega$ Circuit current = $\frac{V_s}{Z} = \frac{25.0}{69.1} = 0.362 \text{ A}$	<ul style="list-style-type: none"> • Correct answer for impedance. • Correct current with incorrect impedance. 	<ul style="list-style-type: none"> • Correct answer for circuit current. 	
(c)	Accept either an impedance phasor diagram or a voltage phasor diagram.  <p>Current is in phase with resistor voltage:</p> $\theta = \tan^{-1}\left(\frac{58.9}{36.0}\right) = 58.6^\circ$ <p>Current leads supply voltage by 58.6°.</p>	<ul style="list-style-type: none"> • Correct phasor diagram. OR Recognition that the circuit current is in phase with the resistor voltage. OR Correct value for phase difference OR States that current leads supply voltage.	<ul style="list-style-type: none"> • Correct value for phase difference as an angle. AND States that current leads supply voltage.	

(d)	<p>Resonance is when the current is a maximum. Current is a maximum when impedance is minimum.</p> <p>This happens when $X_c = X_L$ and $Z = R$ and $V_s = V_R$.</p> <p>So an inductor whose reactance is the same as that of the capacitor should be added to the circuit in order to bring this circuit to resonance.</p>	<ul style="list-style-type: none"> • ONE condition for resonance. 	<ul style="list-style-type: none"> • ONE error in answer. 	<ul style="list-style-type: none"> • Correct answer.
-----	--	--	--	---

NØ	N1	N2	A3	A4	M5	M6	E7	E8
No response; no relevant evidence.	1a	2a	3a	4a	1a + 2m	1a + 3m or	2a + 1m + 1e	1a + 2m + 1e

Q	Evidence	Achievement	Merit	Excellence
TWO (a)	$I_{\max} = \frac{V_s}{R} = \frac{12.0}{22.0} = 0.545 \text{ A}$ <p>Current after two time constants = $I = I_{\max} (1 - e^{-2})$</p> $I = 0.545(1 - e^{-2}) = 0.471 \text{ A}$	<ul style="list-style-type: none"> • Correct value for maximum current. <p>OR</p> <ul style="list-style-type: none"> • Identifies that current changes by 63%. 	<ul style="list-style-type: none"> • Correct answer of 0.471 A. 	
(b)	$V_L = 0, V_R = 12 \text{ V}$	<ul style="list-style-type: none"> • BOTH correct. 		
(c)	$V = \frac{L\Delta I}{t}$ $I = \frac{V}{R} = \frac{12.0}{22.0} = 0.545 \text{ A}$ $V = \frac{1.60 \times 0.545}{2.50 \times 10^{-2}} = 34.9 \text{ V}$ <p>Since the induced voltage opposes the change in current, it will try to prevent the current from decreasing and so will act in the same direction as the source voltage.</p>	<ul style="list-style-type: none"> • Correct value of induced voltage. <p>OR</p> <ul style="list-style-type: none"> • Correct direction of induced voltage 	<ul style="list-style-type: none"> • Correct value of induced voltage. <p>AND</p> <ul style="list-style-type: none"> • Correct direction of induced voltage 	
(d)	<p>If the resistance was changed to 44.0Ω, then the size of the maximum current once it was steady would halve, since $I = \frac{V}{R}$.</p> <p>The increased resistance will have an effect on the time constant as $\tau = \frac{L}{R}$, so time constant would halve. Hence it will take less time for the current to become steady.</p> <p>Since the energy stored in the inductor $E_p = \frac{1}{2} LI^2$, and the current has halved, the energy stored in the inductor once the current is steady would be $\frac{1}{4}$.</p> <p>Evidence can be taken from calculations to support explanation.</p>	<ul style="list-style-type: none"> • Any ONE of: <ul style="list-style-type: none"> - current decreases - time constant decreases - less energy stored in the inductor. 	<ul style="list-style-type: none"> • Any TWO statements with correct reasoning: <ul style="list-style-type: none"> - Current decrease since $I = \frac{V}{R}$, and R has doubled. - Time constant decreases because R has increased. - Less energy is stored in the inductor as current has decreased and energy stored $= \frac{1}{2} LI^2$. 	<ul style="list-style-type: none"> • Current and time constant have halved with reasons including reasoning out the energy stored in the inductor has decreased by $\frac{1}{4}$ of its original value.

NØ	N1	N2	A3	A4	M5	M6	E7	E8
No response; no relevant evidence.	1a	2a	3a	4a	1a + 2m	1a + 3m	2a + 1m + 1e	1a + 2m + 1e

Q	Evidence	Achievement	Merit	Excellence
THREE (a)	$C = \frac{\epsilon_0 \epsilon_r A}{d} = \frac{8.85 \times 10^{-12} \times 1.00 \times 0.16}{0.001} = 1.42 \times 10^{-9} \text{ F}$	<ul style="list-style-type: none"> • Correct working. *This is a SHOW THAT question. 		
(b)	<p>Energy stored</p> $= \frac{1}{2} CV^2 = \frac{1}{2} \times 1.42 \times 10^{-9} \times 9.00^2$ $= 5.75 \times 10^{-8} \text{ J}$ <p>Introducing a dielectric will allow more charge to be stored on the plates, thereby increasing the capacitance 7 times.</p> <p>So, the energy stored will increase 7 times.</p>	<ul style="list-style-type: none"> • Correct energy stored. OR Energy increases 7 times. 	<ul style="list-style-type: none"> • Correct energy stored AND Capacitance increases 7 times, so energy stored increases 7 times. 	
(c)	<p>The charge on the plates remains the same. However, Capacitance, C, decreases as distance, d, between the plates increases $C = \frac{Q}{V}$. So, the voltage across the plates increases.</p>	<ul style="list-style-type: none"> • One correct statement. 	<ul style="list-style-type: none"> • Two statements with one correct reason. 	
(d)	<p>Total capacitance = $\frac{1}{C_T} = \frac{1}{470 \mu\text{F}} + \frac{1}{800 \mu\text{F}}$</p> <p>$C_T = 296 \mu\text{F}$</p> <p>Total charge = $Q_T = C_T V = 296 \times 10^{-6} \times 12$</p> <p>$= 3.552 \times 10^{-3} \text{ C}$</p> <p>Voltage across 470 μF capacitor:</p> $V = \frac{Q}{C} = \frac{3.552 \times 10^{-3}}{470 \times 10^{-6}} = 7.56 \text{ V}$	<ul style="list-style-type: none"> • Total capacitance. OR Total charge with incorrect capacitance. 	<ul style="list-style-type: none"> • Total charge. OR One error in calculation. 	<ul style="list-style-type: none"> • Correct answer for voltage.

NØ	N1	N2	A3	A4	M5	M6	E7	E8
No response; no relevant evidence.	1a	2a	3a	4a	1a + 2m	1a + 3m	2a + 1m + 1e	1a + 2m + 1e

Cut Scores

Not Achieved	Achievement	Achievement with Merit	Achievement with Excellence
0 – 7	8 – 13	14 – 18	19 – 24