

3

91526



NEW ZEALAND QUALIFICATIONS AUTHORITY
MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD
KĪA NOHO TAKATŪ KI TŌ ĀMUA AO!

SUPERVISOR'S USE ONLY

Level 3 Physics, 2016

91526 Demonstrate understanding of electrical systems

2.00 p.m. Tuesday 15 November 2016
Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3-PHYSR.

In your answers use clear numerical working, words and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–8 in the correct order and that none of these pages is blank.


YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.

TOTAL

ASSESSOR'S USE ONLY

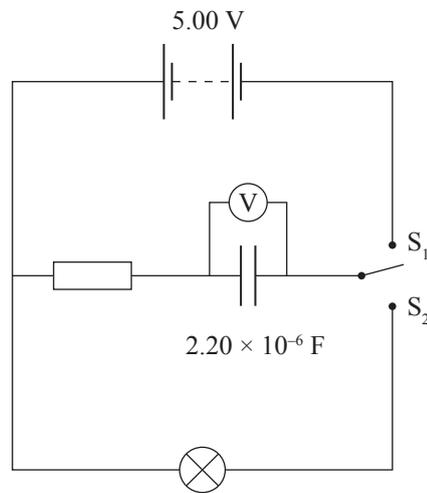
QUESTION ONE: CHARGING A CAPACITOR

Eleanor sets up a circuit to investigate how capacitors operate. The circuit is shown below. The circuit includes a 2.20×10^{-6} F capacitor and a double pole switch.



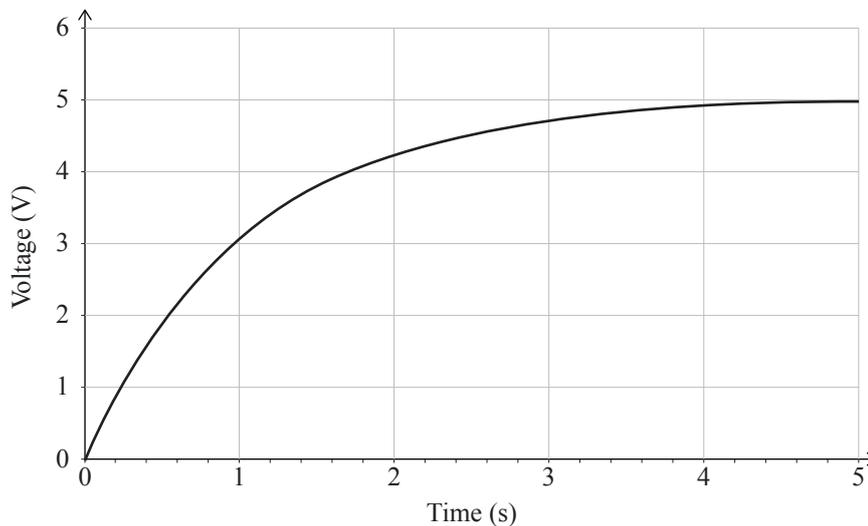- (a) Calculate the maximum charge stored by the capacitor in this circuit.

The capacitor is initially uncharged, and the switch is in the position shown. Eleanor moves the switch to S_1 and the capacitor charges up. A graph of the capacitor voltage against time is shown below.



- (b) Use the graph to calculate the resistance of the resistor.
Draw lines on the graph to help explain your working.

QUESTION TWO: THE TRANSFORMER

Transformers can be used to increase or decrease the size of an AC voltage. Wei has a transformer that is designed to convert 240 V into 12.0 V.


The secondary coil has 40 turns.

- (a) Calculate the number of turns on the primary coil.

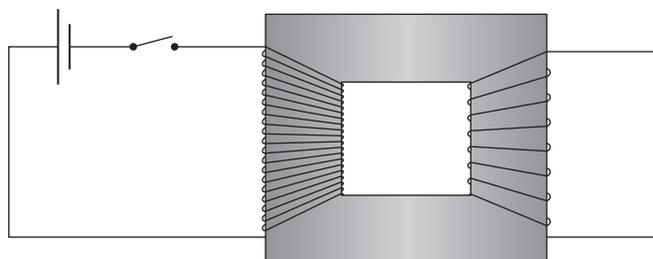- (b) Explain how an alternating voltage across the primary coil creates an alternating current in a light bulb connected to the secondary coil.

Each coil of a transformer acts as an inductor.


A primary coil is attached to a battery and switch as shown in the diagram below. The switch is closed and then some time later the switch is opened.



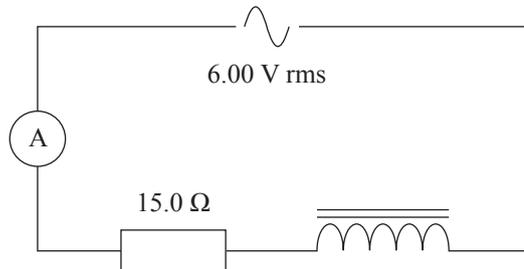QUESTION THREE: MEASURING IRON IN SAND

Vivienne wants to measure the amount of iron in iron-sand mixtures collected from different beaches. The diagram below shows the circuit that she uses. The circuit includes a 500-turn coil with a resistance of $15.0\ \Omega$, and an AC supply.

The coil behaves like a resistor and an inductor in series.



The coil has a hollow core that is initially empty. Vivienne adjusts the power supply voltage to 6.00 V rms.

- (a) Calculate the instantaneous maximum (peak) voltage across the power supply.

During testing, Vivienne puts a mixture of iron and sand inside the core of the coil.

- (b) State what effect this has on the size of the coil's reactance.

With reference to impedance, explain what happens to the size of the current in the circuit as she adds the mixture of iron and sand.
