

No part of the candidate evidence in this exemplar material may be presented in an external assessment for the purpose of gaining credits towards an NCEA qualification.

3

91526



915260



NEW ZEALAND QUALIFICATIONS AUTHORITY
MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD
KIA NOHO TAKATŪ KI TŌ ĀMUA AO!

SUPERVISOR'S USE ONLY

Level 3 Physics, 2016

91526 Demonstrate understanding of electrical systems

2.00 p.m. Tuesday 15 November 2016
Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3-PHYSR.

In your answers use clear numerical working, words and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–8 in the correct order and that none of these pages is blank.

YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.

Excellence


TOTAL

23

ASSESSOR'S USE ONLY

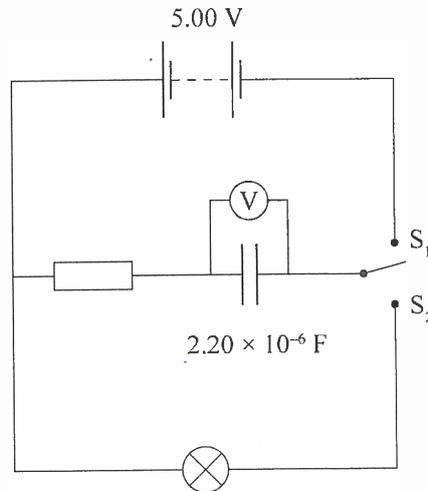QUESTION ONE: CHARGING A CAPACITOR

Eleanor sets up a circuit to investigate how capacitors operate. The circuit is shown below. The circuit includes a 2.20×10^{-6} F capacitor and a double pole switch.




- (a) Calculate the maximum charge stored by the capacitor in this circuit.

$$Q = CV = 2.2 \times 10^{-6} \times 5 = 1.1 \times 10^{-5} \text{ C}$$



CA

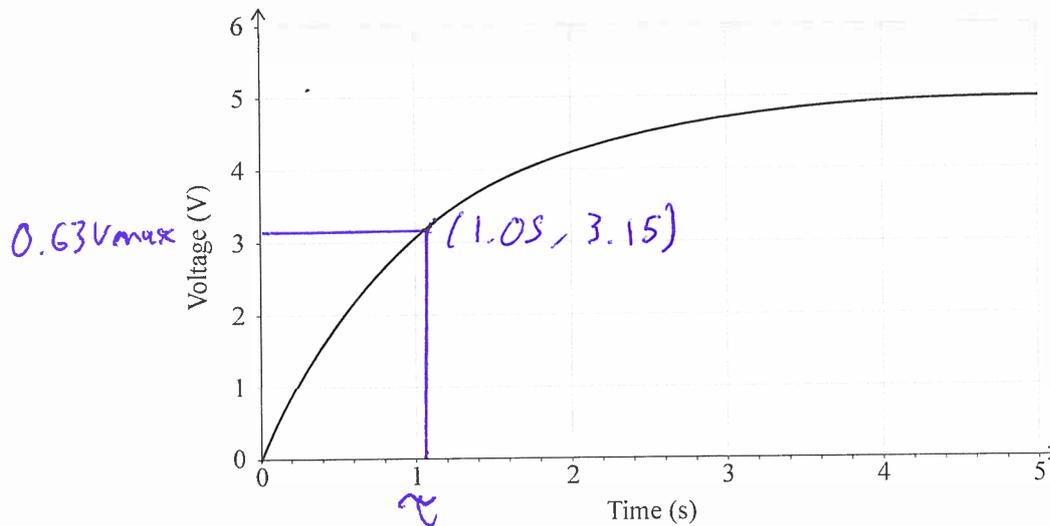The capacitor is initially uncharged, and the switch is in the position shown. Eleanor moves the switch to S_1 and the capacitor charges up. A graph of the capacitor voltage against time is shown below.



- (b) Use the graph to calculate the resistance of the resistor.

Draw lines on the graph to help explain your working.

$$0.63 \times 5 = 3.15, \quad \tau \approx 1.05 \text{ s}$$

$$R = \frac{\tau}{C} = \frac{1.05}{2.2 \times 10^{-6}} = 477000 \, \Omega \quad (3 \text{ sf})$$



N

QUESTION TWO: THE TRANSFORMER

Transformers can be used to increase or decrease the size of an AC voltage. Wei has a transformer that is designed to convert 240 V into 12.0 V.

The secondary coil has 40 turns.

- (a) Calculate the number of turns on the primary coil.

$$\frac{N_p}{N_s} = \frac{V_p}{V_s}, \quad N_p = 40 \left(\frac{240}{12} \right)$$


$$N_p = 800$$

- (b) Explain how an alternating voltage across the primary coil creates an alternating current in a light bulb connected to the secondary coil.

The alternating voltage causes an alternating ~~current~~ which ~~the~~ changes the flux in the primary coil. There will be a ~~an~~ back-emf induced in the primary coil to oppose the changing flux. This ^{back-} emf in the primary coil ~~is~~ is changing, so it will induce an alternating current in the secondary coil, which in turn ~~induces~~ causes an alternating current in the bulb.


Each coil of a transformer acts as an inductor.

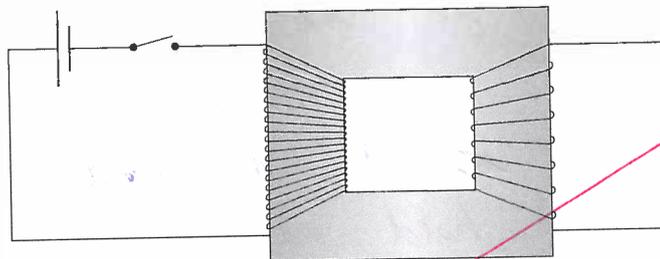A primary coil is attached to a battery and switch as shown in the diagram below. The switch is closed and then some time later the switch is opened.



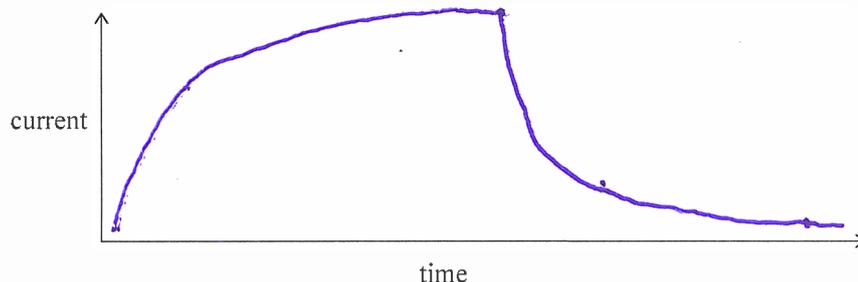- (c) Sketch a graph showing how the current in the coil changes when the switch is closed and then some time later is opened.

Give a comprehensive explanation for the shape of your graph.



If you need to redraw your response, use the graph on page 8.

When the switch is closed, there is an ~~instant~~ increase in current, which ~~causes~~ causes a changing flux ~~in~~ in the 'inductor' which it will act to oppose by producing a back-EMF. The current will still increase to maximum, but at a lesser rate than it would without the inductor, which is why ~~the graph increases but at a lesser rate~~ shown on the graph (it would increase to I_{max} almost instantaneously without the inductor). ~~It is curved because there is less potential difference as the current increases.~~
After the switch is opened, the opening
cont.

- (d) Calculate the energy stored in the primary coil's magnetic field when the switch has been closed for several seconds.

battery voltage = 6.0 V

resistance of primary coil = 35 Ω

inductance of primary coil = 0.10 H

$$E = \frac{1}{2} L I^2 = 0.5 \times 0.1 \times I^2$$

$$I = \frac{V}{R} = \frac{6}{35} = 0.17 \text{ A}$$

$$E = \frac{1}{2} \times 0.5 \times 0.1 \times 0.17^2$$


$$E = 6.5 \times 10^{-3} \text{ J (2sf)}$$



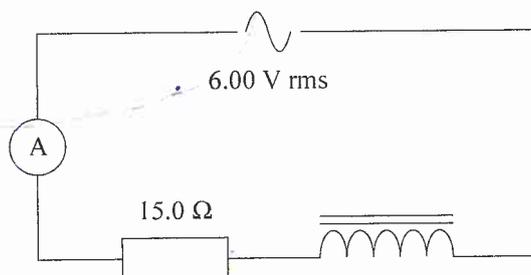QUESTION THREE: MEASURING IRON IN SAND

Vivienne wants to measure the amount of iron in iron-sand mixtures collected from different beaches. The diagram below shows the circuit that she uses. The circuit includes a 500-turn coil with a resistance of 15.0Ω , and an AC supply.

The coil behaves like a resistor and an inductor in series.



The coil has a hollow core that is initially empty. Vivienne adjusts the power supply voltage to 6.00 V rms.

- (a) Calculate the instantaneous maximum (peak) voltage across the power supply.

$$U_{\max} = \sqrt{2} V_{\text{rms}} = \sqrt{2} \times 6 = 8.49 \text{ V (3sf)}$$



a

During testing, Vivienne puts a mixture of iron and sand inside the core of the coil.

- (b) State what effect this has on the size of the coil's reactance.

With reference to impedance, explain what happens to the size of the current in the circuit as she adds the mixture of iron and sand.


The inductance of the coil increases as the iron contributes to ~~the~~ increasing the flux. This causes ^{reactance} ~~impedance~~ to increase ($X_L = \omega L$), which increases the impedance of the circuit. Impedance ^{acts} ~~is~~ like ~~resistance~~ resistance in DC, so the size of the current decreases ~~the~~ ($I = \frac{V}{Z}$)



M

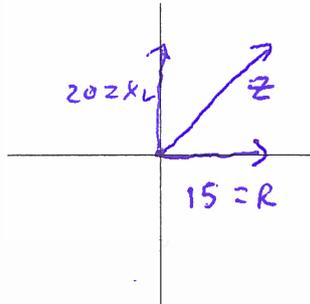- (c) When Vivienne sets the frequency of the current to 1.00×10^3 Hz, the inductance of the coil is 3.18×10^{-3} H.

Using a phasor diagram or otherwise, calculate the size of the rms current in the circuit.



$$\omega = 2\pi f = 2000\pi \text{ rads}^{-1}$$

$$X_L = \omega L = 2000\pi \times 3.18 \times 10^{-3}$$

$$X_L = 20.0 \Omega \text{ (3sf)}$$

$$Z = \sqrt{15^2 + 20^2} = 25 \Omega \text{ (from vector)}$$

$$I = \frac{V}{Z} = \frac{6}{25} = 0.24 \text{ A}$$

- (d) Vivienne adds a capacitor in series with the coil, and finds that the current increases.


Explain why the current increases.

The ~~resistance~~ capacitor has ^{reactance} ~~impedance~~ ($X_C = \frac{1}{\omega C}$).
 This ^{reactance} ~~impedance~~ is 180° out of phase with the inductor ^{reactance} ~~impedance~~, which ~~also~~ means that the two ^{reactances} ~~impedances~~ 'contract' each other.
 This ~~decreases~~ the impedance of the circuit:
 Before: $Z = \sqrt{X_L^2 + R^2}$, After: $Z = \sqrt{(X_L - X_C)^2 + R^2}$

SPARE DIAGRAMS

ASSESSOR'S
USE ONLY

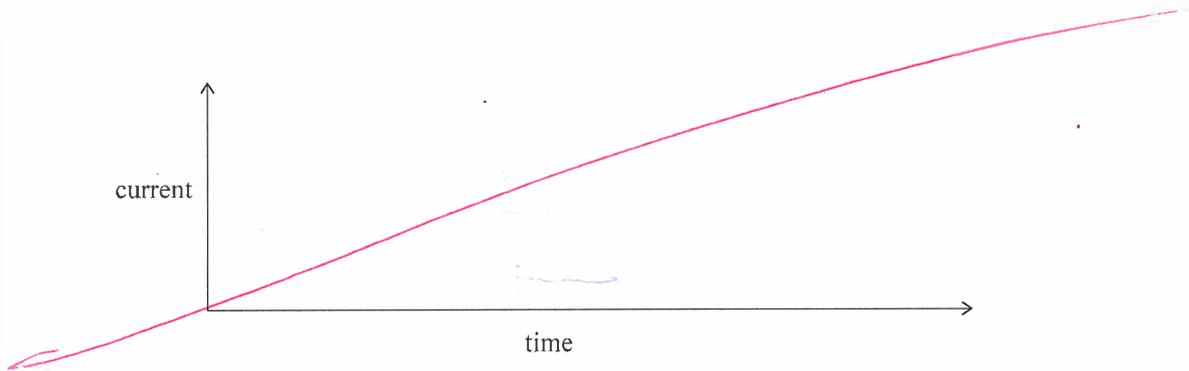If you need to redraw your response to Question Two (d), use the axes below. Make sure it is clear which answer you want marked.



Extra paper if required.

Write the question number(s) if applicable.

QUESTION
NUMBER

91526
2c) acts ~~as~~ as a ^{very} large resistance which causes the flow of current to decrease rapidly. The inductor acts to oppose this change by producing an induced voltage which acts to increase the current. The value of the current ~~event~~ shrinks to 0 ~~after about 5 time constants~~, but at a slower rate due to the induced voltage opposing the change.

3d) which causes the current to increase ($I = \frac{V}{R}$).