

No part of the candidate evidence in this exemplar material may be presented in an external assessment for the purpose of gaining credits towards an NCEA qualification.

3

SUPERVISOR'S USE ONLY



NEW ZEALAND QUALIFICATIONS AUTHORITY
MANA TOHU MĀTAURANGA O AOTEAROA

Level 3 Physics, 2014

91526 Demonstrate understanding of electrical systems

2.00pm Tuesday 25 November 2014
Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3-PHYSR.

In your answers use clear numerical working, words and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–8 in the correct order and that none of these pages is blank.

YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.

Excellence


TOTAL

24

ASSESSOR'S USE ONLY

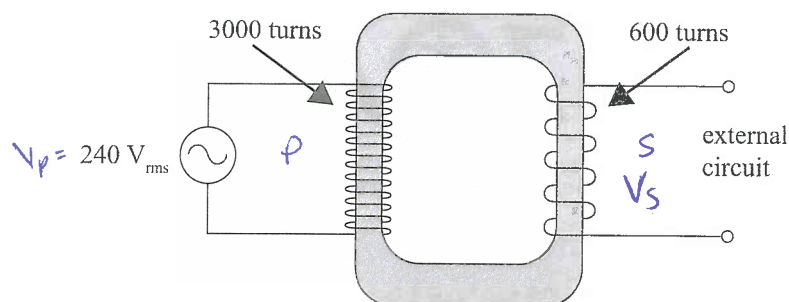QUESTION ONE: AC

The ideal transformer shown below has 3000 turns in its primary coil, and 600 turns in the secondary coil. A $240 \text{ V}_{\text{rms}}$ AC power supply is connected across the primary coil. The secondary coil is connected to an external circuit.



- (a) (i) Calculate the rms voltage across the external circuit.

$$\frac{N_P}{N_S} = \frac{V_P}{V_S} \quad V_S = \frac{240}{(3000/600)}$$

$$\frac{3000}{600} = \frac{240}{V_S} \quad = 48.0 \text{ V (2sf).}$$

- (ii) Calculate the peak voltage across the external circuit.

$$V_{\text{peak}} = \sqrt{2} \times V_{\text{rms}} \quad V_{\text{peak}} = 68.0 \text{ V (2sf).}$$

$$= \sqrt{2} \times 48$$


$$= 67.89 \text{ V.}$$

- (b) Explain why rms values are often used to describe AC voltages.


RMS voltages are used as in an AC circuit the voltage constantly changes. The RMS value indicates the voltage which would give the same power output as the equivalent DC circuit. (with peak voltage of the supply in the DC circuit). In this sense the rms voltage gives an 'average' voltage & power output for the AC circuit.

correct explanation

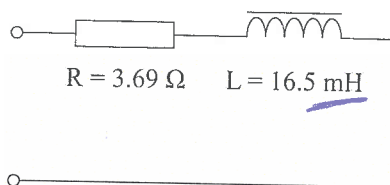- (c) The external circuit consists of a resistor and an inductor as shown. The frequency of the power supply is 50.0 Hz.



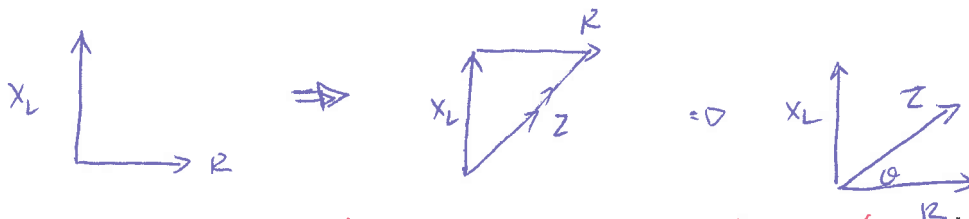By drawing a phasor diagram, show how the impedance of the external circuit can be calculated.



Correct phasor diagram, explanation & calculation

The impedance can be calculated by vectorially adding inductor impedance X_L and resistor R in the circuit, as they are out of phase.

due to changing voltage & current

Hence as X_L leads the circuit resistance R by 90° or $\frac{1}{4}\pi$,


Z is the sum of these vectors. Hence $Z = \sqrt{X_L^2 + R^2}$

where $X_L = 2\pi fL$ and $R = 3.69 \Omega$.

$$X_L = 2\pi \times 50 \times 16.5 \times 10^{-3} = 5.18 \Omega \quad \therefore Z = \sqrt{5.18^2 + 3.69^2} = 6.36 \Omega$$

$\therefore Z$ will lead R by θ , and is in phase with neither X_L or R .

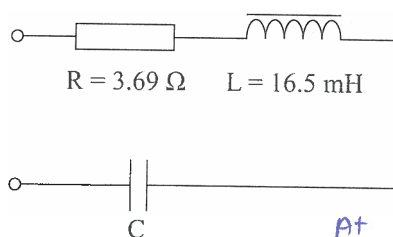- (d) A capacitor is added to the external circuit, causing the circuit to be at resonance.



At resonance $X_C = X_L$.

At resonance $V_C \neq V_L = 0$.

$V_{\text{circuit}} = V_R$

Determine the rms voltage across the capacitor.

$$\frac{1}{2\pi fC} = 2\pi fL$$

$$= 2 \times \pi \times 50 \times 16 \times 10^{-3}$$

$$\frac{1}{2\pi \times 50C} = 5.183627878 \Omega = X_C$$

$$100\pi C = 0.192915$$

$$C = 6.14 \times 10^{-4} \text{ F}$$

At resonance $Z = \sqrt{(X_C - X_L)^2 + R^2}$

$$X_C - X_L = 0$$

$$Z = R$$

$$= 3.69 \Omega$$

$$\therefore V_C = V_L$$

$$I = \frac{V_{\text{rms}}}{Z} = \frac{48}{3.69} = 13.008 \text{ A}$$

$$V_C = I X_C$$

$$= 13.008 \times 5.183627878$$


$$= 67.43 \text{ V}$$

$$V_C = 67.4 \text{ V}_{\text{rms}} \quad (3 \text{ sf})$$

QUESTION TWO: BATTERIES

ASSESSOR'S
USE ONLY

$$R_T = 2.70 + 5.00 + 20.0 + 2.50$$

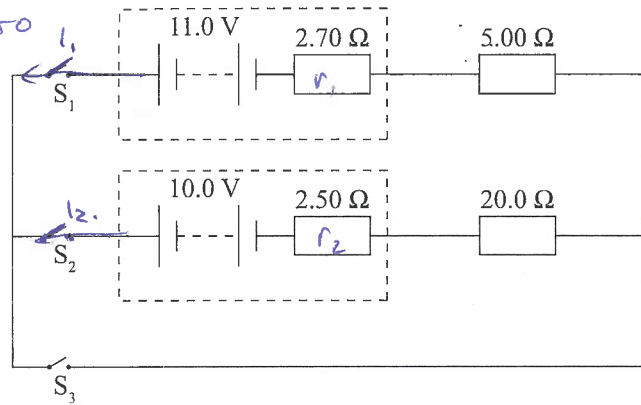

The circuit diagram shows two batteries connected into a circuit. The internal resistance, r_1 , of the 11.0 V battery is 2.70Ω , and the internal resistance, r_2 , of the 10.0 V battery is 2.50Ω .

- (a) Switches S_1 and S_2 are closed and switch S_3 is left open.

Show that the current in the circuit is 0.0331 A .

$$\text{Opposing voltages} = 11 - 10 \rightarrow V_{\text{Total}} = 1.0 \text{ V.}$$

$$\text{Total resistance in circuit} = 5.0 + 2.70 + 20.0 + 2.50 = 30.2 \Omega$$

$$V = IR$$

$$I = \frac{V}{R}$$

$$= \frac{1.0}{30.2}$$

$$= 0.03311258278 \text{ A}$$

$$= 0.0331 \text{ A (3 sf)}$$

correct calculation

- (b) In which direction will the current be flowing through switch S_1 ?

Explain your answer.

The current produced by the 11 V battery will flow anticlockwise through the switch S_1 and will be opposed by the current from the 10 V battery flowing clockwise through S_2 . However, as the remaining voltage from the opposing 11 V and 10 V sources is 1 V anticlockwise, the current will also flow in this direction hence the current will flow anticlockwise through the switch S_1 (to the left).

correct direction
& reason

- (c) Switch S_3 is now closed so all three switches are closed.

Show, using Kirchhoff's laws, that the current through switch S_3 is 1.87 A.

ASSESSOR'S
USE ONLY

~~By Kirchhoff's second law around outer loop = 0~~ $V_{\text{outer loop}}$

$$\therefore 11 - 270 I_1 - 5 \times I_1 = 0 \quad 11 - (2.7) I_1 - 5 \times I_1 = 0$$

$$11 = 7.7 I_1$$

$V_{\text{inner loop}}$

$$10 - (2.50 \times I_2) - (20 \times I_2) = 0$$

$$10 = 22.5 I_2$$

$$I_1 = \frac{11}{7.7} = 1.42857 \text{ A}$$

$$I_2 = \frac{10}{22.5} = 0.4444 \text{ A}$$

correct
working

m

$$\text{Current in to } S_3 \text{ junction} = I_1 + I_2$$

$$I_1 + I_2 = 0.0331 \text{ A}$$

$$\therefore I_1 = 0.0331 + I_2$$

$$\therefore 11 - 2.7(0.0331 + I_2) - 5(0.0331 + I_2) = 0 \quad I_{S_3} = I_1 + I_2 = 0.4444 + 1.42857$$

$$I_{S_3} = 1.87 \text{ A (3sf)}$$

- (d) Switch S_1 is now opened, leaving switches S_2 and S_3 closed. After this circuit has been operating for some time, the 10.0 V battery starts to go flat. A student suspects that this is caused by an increase in the internal resistance.

Explain what effect a changing internal resistance has on the power delivered to the 20.0 Ω resistor.

A full answer will include some sample calculations.

Internal resistance is caused by a resistance in the chemical reactions occurring in the battery, causing energy to be lost by charge passing through the battery and hence reducing the voltage and current provided to the external circuit (As $V=IR$ and R_{circuit} is constant). Because both the voltage and the current delivered to the circuit decrease when the internal resistance is higher, this results in a smaller power through the 20 Ω resistor, which receives the full remaining current and voltage. ($P=VI$) \therefore if both V and I decrease, P will decrease.

e.g. Internal resistance of 3 Ω

$$I_{\text{circuit}} = \frac{10}{(2.5 + 20)} = 0.43 \text{ A}$$

$$\therefore V_{\text{circuit}} = \text{EMF} - (0.44 \times 3.0) = 8.67 \text{ V}$$

$$I_{\text{circuit}} = \frac{8.67}{20} = 0.43 \text{ A}$$

$$P = 8.67 \times 0.43 = 3.72 \text{ W (3sf)}$$

NORMAL

IR of 2.5 Ω

$$I = \frac{10}{(2.5 + 20)} = 0.44 \text{ A}$$

$$V_c = \text{EMF} - (0.44 \times 2.5) = 8.9$$


$$I_c = \frac{8.9}{20} = 0.45 \text{ A}$$

$$P = 8.9 \times 0.45 = 3.96 \text{ W (3sf)}$$

emf constant
 $V, I \& P$
decreases

Eg

QUESTION THREE: ENERGY

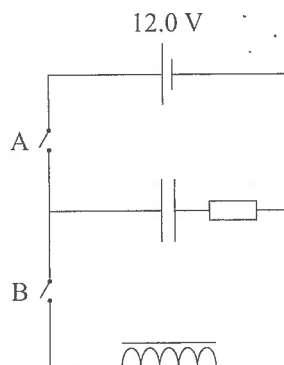ASSESSOR'S
USE ONLY

- (a) In the circuit above, switch B is kept open and switch A is closed, allowing charge to flow onto the plates of the capacitor.

Explain why the voltage of the capacitor rises to the voltage of the battery.

As time passes, charge builds on the capacitor plates as current flows through the circuit and is unable to flow through the capacitor. This results in charge being held on the capacitor plates as one side where charge builds becomes positively charged and (due to attraction of opposite charges) the other side becomes negatively charged. Charge becomes stored here due to this attraction.

- (b) When the capacitor in the circuit above is fully charged, it carries a charge of $8.60 \times 10^{-3} \text{ C}$.


Calculate the energy stored in the capacitor when it is fully charged.

$E = \frac{1}{2} QV$ $E = 0.052 \text{ J (3sf)}$
 $= \frac{1}{2} 8.6 \times 10^{-3} \times 12$ Correct calculation
 $= 0.0516 \text{ J.}$

(cont. part a)

and reduces the amount of charge and energy the charge has and prevents it from passing around the circuit. The voltage of the capacitor therefore opposes the voltage of the supply and cannot exceed the supply voltage due to Kirchhoff's law (voltage around a loop sums to 0) and the capacitor holds all charge in the circuit on its plates with $V_C = V_S$.

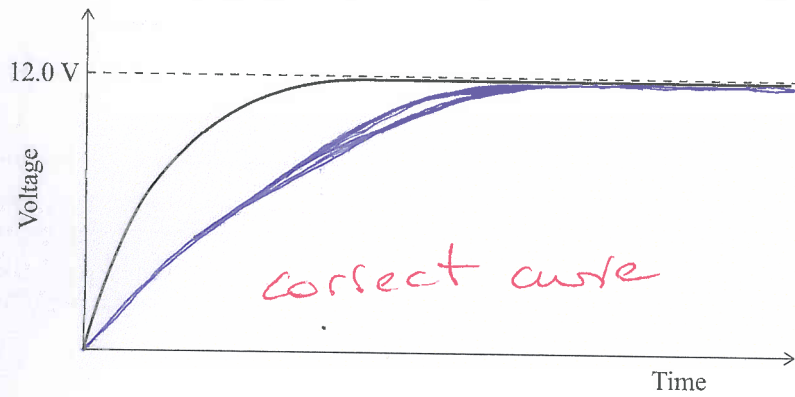- (c) The graph below shows the relationship between voltage and time as the capacitor charges.



Sketch another curve on the graph to show the effect of an increased resistance on the charging of the capacitor.

Now switch A is opened and switch B is closed. The current changes with time.

- (d) Explain the effect that inductors have on currents that change with time.

A changing current through an inductor coil creates an opposing ^{changing} magnetic flux through the coil. This results in an induced voltage which acts to oppose the change in current and flux through the coil. The size of this induced voltage is directly proportional to the rate at which the current is changing. When switch B is first closed there is an increasing current

through the coil from the supply voltage, producing an opposing induced inductor voltage through the inductor which opposes the $\Delta I / \Delta t$ and therefore opposes the supply voltage. (no reference to increasing the time it takes)

- (e) Discuss how energy is stored in the capacitor and inductor at the instant switch B is closed, and then while the capacitor is discharging.

→ and the capacitor discharges
When switch B is closed the stored energy in the capacitor is released -

it does not store more energy. This energy is released as electrical

energy as charge flows off the capacitor plates. This increases

the current flowing through the inductor creating a changing

magnetic flux through the coil which in turn allows energy to

be stored in the magnetic field in the coil as the voltage in the coil opposes the changing current through the coil.

When switch B is closed there is a lot of energy stored due to the extremely high induced voltage in the coil (without V supply V induced can be huge → no Kirchhoff law).

In the capacitor electrical potential energy is stored in the electric field between the plates (this decreases as it charges) and in the inductor the energy is stored in the magnetic field created by an increasing changing current or electrical potential energy which creates a magnetic flux.

a

m

e

Eg