

3

91526



NEW ZEALAND QUALIFICATIONS AUTHORITY
MANA TOHU MĀTAURANGA O AOTEAROA

QUALIFY FOR THE FUTURE WORLD
KIA NOHO TAKATŪ KI TŌ ĀMUA AO!

SUPERVISOR'S USE ONLY

Level 3 Physics, 2018

91526 Demonstrate understanding of electrical systems

2.00 p.m. Tuesday 20 November 2018
Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

You should attempt ALL the questions in this booklet.

Make sure that you have Resource Booklet L3-PHYSR.

In your answers use clear numerical working, words, and/or diagrams as required.

Numerical answers should be given with an SI unit, to an appropriate number of significant figures.

If you need more room for any answer, use the extra space provided at the back of this booklet.

Check that this booklet has pages 2–12 in the correct order and that none of these pages is blank.


YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.

TOTAL

ASSESSOR'S USE ONLY

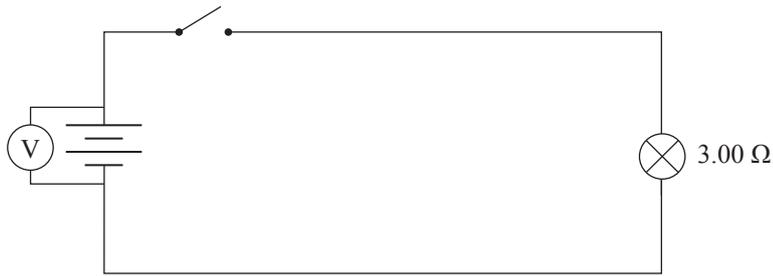QUESTION ONE

Casey sets up a battery, a switch, and a $3.00\ \Omega$ light bulb in series.




The battery voltage is measured to be $6.02\ \text{V}$ when the switch is open. However, when the switch is closed, Casey notices that the battery voltage drops to $5.85\ \text{V}$.

- (a) Explain why the battery voltage is less when the switch is closed.

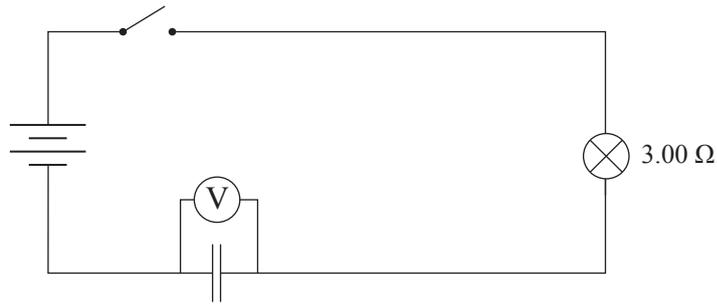
- (b) Casey measures the current through the circuit to be $1.89\ \text{A}$.

State the EMF, and show that the internal resistance of the battery is approximately $0.09\ \Omega$.

Casey now adds a capacitor in series with the battery and closes the switch. Casey measures the voltage across the capacitor as it charges.




Capacitor Voltage during Charging

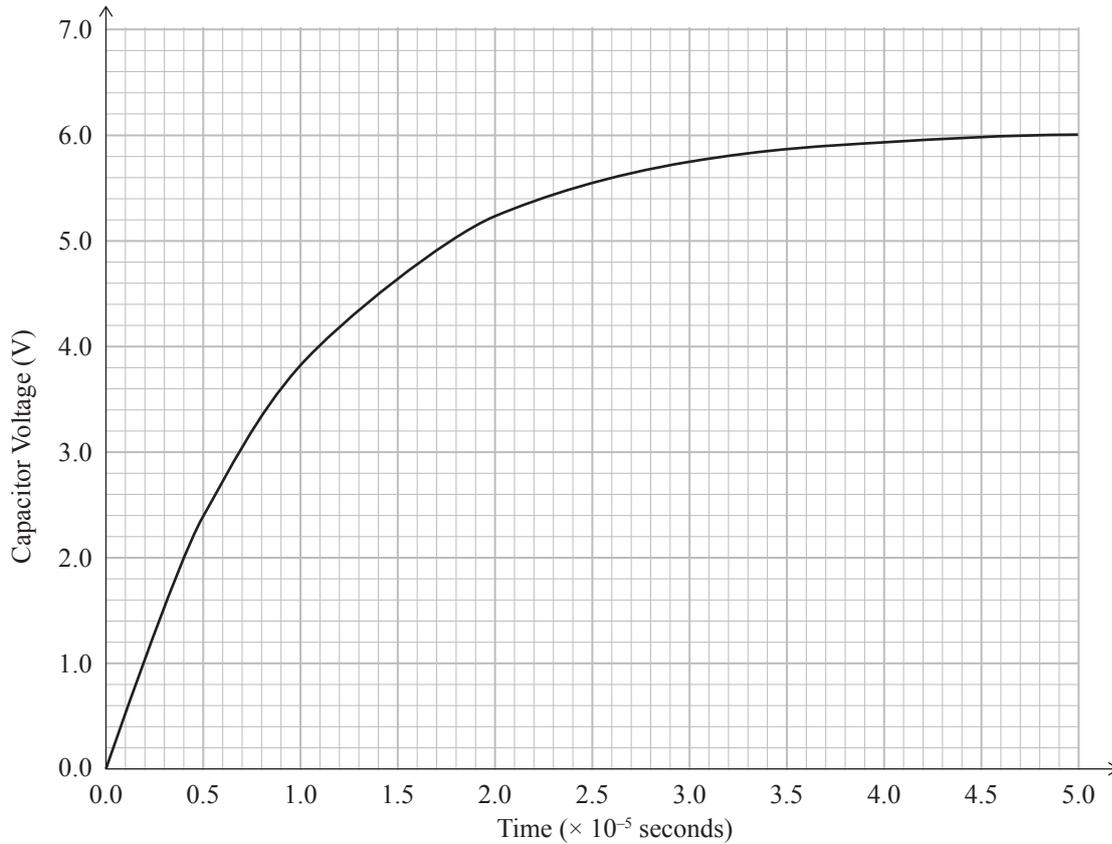

- (c) Using information from the graph, determine the capacitance of the capacitor.

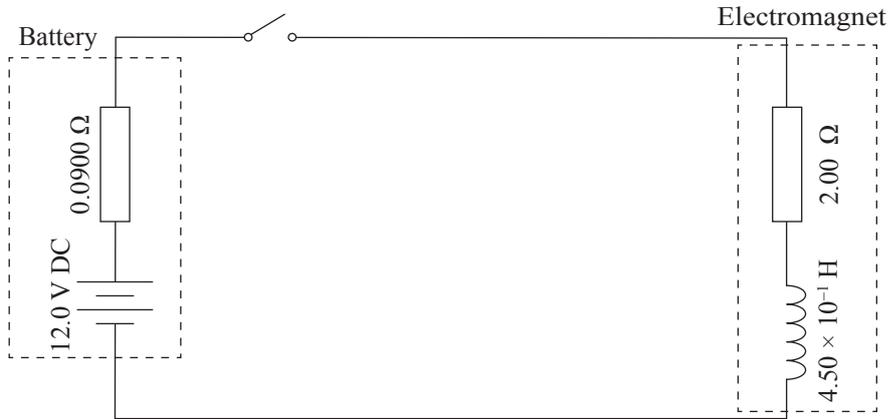QUESTION TWO

Casey is using an electromagnet that has an inductance of $4.50 \times 10^{-1} \text{ H}$ and a resistance of $2.00 \ \Omega$. Casey connects it to a 12.0 V DC battery with an internal resistance of $0.0900 \ \Omega$.




- (a) Determine the current through the electromagnet a few minutes after the switch is closed.

- (b) Casey opens the switch and a large spark jumps across the terminals of the open switch.

Explain how the coil can produce such a high voltage when the switch is opened.

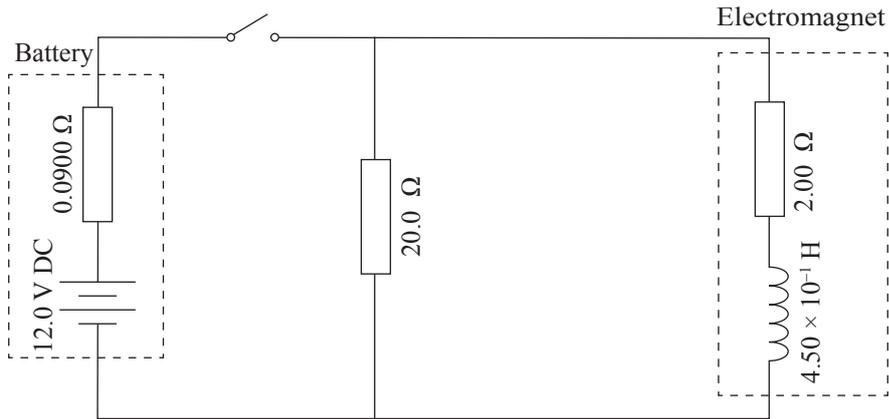- (c) To prevent damaging sparks, Casey places a $20.0\ \Omega$ resistor in parallel with the electromagnet.




At one point, shortly after the switch is closed, the rising current drawn from the battery has reached $2.00\ \text{A}$ and a back EMF of $9.00\ \text{V}$ has been induced across the inductor.

Show that the current through the electromagnet at this time is $1.41\ \text{A}$.

(d) After many more minutes, the current through the coil is a steady 5.72 A.

The switch is now opened.

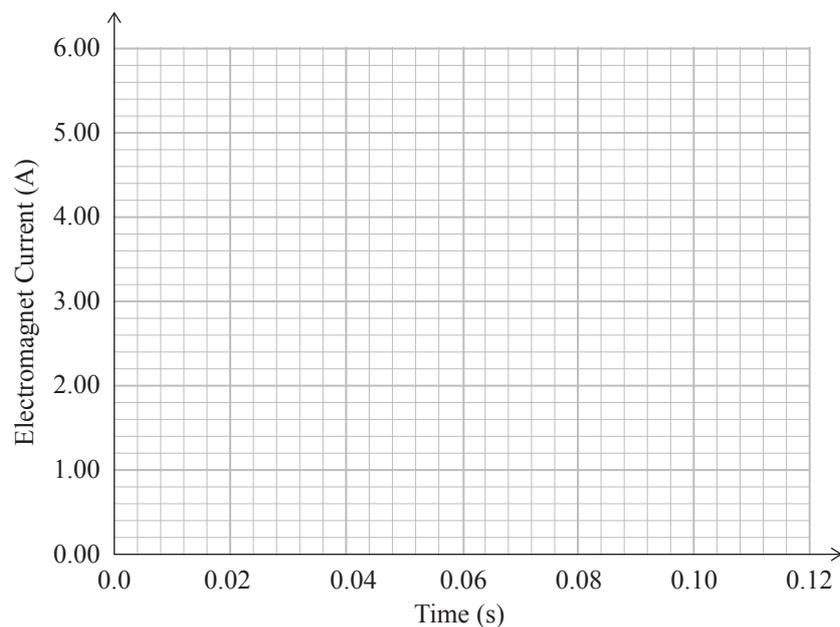(i) Plot the graph of current versus time for the electromagnet as the current falls to zero.



(ii) Explain how the presence of the $20\ \Omega$ resistor protects against the high voltage sparks that Casey witnessed earlier.

QUESTION THREE

Casey is experimenting with building inductors and capacitors.


To make a capacitor, Casey places a thin layer of rubber between two 1.20 m^2 aluminium plates, and then squeezes the sheets together. The rubber has a dielectric constant of 8.90 and is compressed to a thickness of $1.00 \times 10^{-4} \text{ m}$.



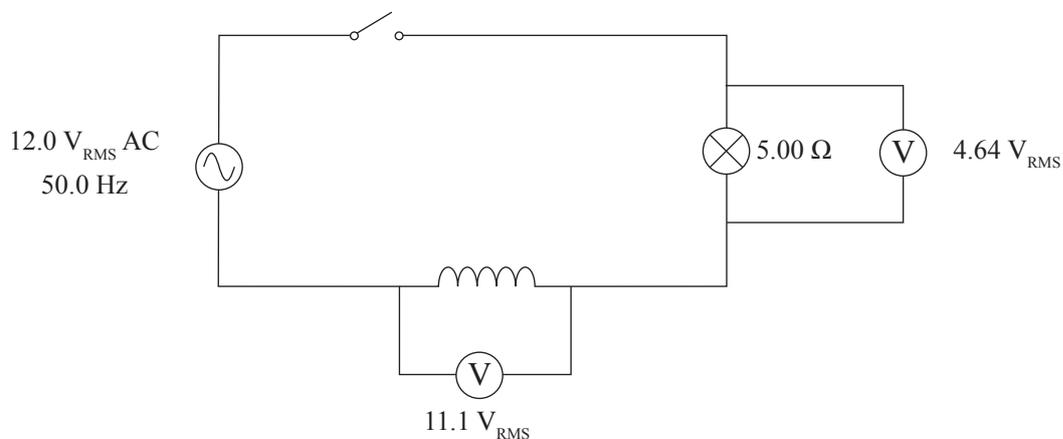- (a) Show that the capacitance of Casey's capacitor is $9.45 \times 10^{-7} \text{ F}$.

To make an inductor, Casey winds several hundred turns of insulated copper wire around an iron rod. Casey wants to test its inductance.

Casey connects the circuit shown below. The voltage across the lamp is measured to be $4.64 \text{ V}_{\text{RMS}}$, and across the inductor to be $11.1 \text{ V}_{\text{RMS}}$.



- (b) Show that the inductance of Casey's inductor is $3.81 \times 10^{-2} \text{ H}$.

Casey adds in the 9.45×10^{-7} F capacitor to create an LCR series circuit. The light bulb barely glows. Casey switches the AC power supply to its maximum frequency setting of 4.00×10^2 Hz.

- (c) Determine the new impedance of the circuit.

- (d) (i) Calculate the resonant frequency for the circuit and compare this with the maximum frequency setting of the power supply.

- (ii) Describe how Casey could physically alter the inductor and capacitor to increase the current through the light bulb using this power supply.
