

SUPERVISOR'S USE ONLY

3

91526



Draw a cross through the box (X) if you have NOT written in this booklet

+



Mana Tohu Mātauranga o Aotearoa  
New Zealand Qualifications Authority

## Level 3 Physics 2025

### 91526 Demonstrate understanding of electrical systems

Credits: Six

Achievement	Achievement with Merit	Achievement with Excellence
Demonstrate understanding of electrical systems.	Demonstrate in-depth understanding of electrical systems.	Demonstrate comprehensive understanding of electrical systems.

Check that the National Student Number (NSN) on your admission slip is the same as the number at the top of this page.

**You should attempt ALL the questions in this booklet.**

Make sure that you have Resource Booklet L3–PHYSR.

In your answers use clear numerical working, words, and/or diagrams as required.

Numerical answers should be given with an appropriate SI unit.

If you need more room for any answer, use the extra space provided at the back of this booklet.


Check that this booklet has pages 2–12 in the correct order and that none of these pages is blank.

Do not write in the margins (✂✂✂). This area will be cut off when the booklet is marked.

**YOU MUST HAND THIS BOOKLET TO THE SUPERVISOR AT THE END OF THE EXAMINATION.**
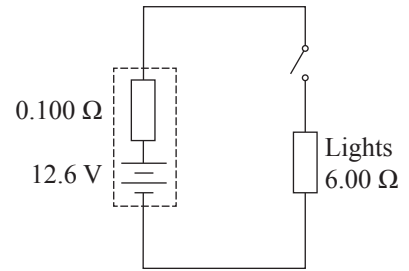
### QUESTION ONE: DC CIRCUITS

Mereana has a caravan, which has a simple battery-powered circuit for the lighting with a total resistance of  $6.00\ \Omega$ . The battery has an EMF of  $12.6\ \text{V}$ , and an internal resistance of  $0.100\ \Omega$ .



- (a) When the switch is closed, the current from the battery is  $2.07\ \text{A}$ .

Show that the terminal voltage of the battery is  $12.4\ \text{V}$ .

---



---



---

- (b) As the battery is used over time, its internal resistance will increase.

Explain the effect that this will have on the terminal voltage of the battery.

---



---



---




---



---

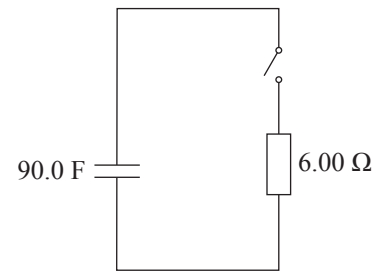- (c) Mereana is investigating using a capacitor to power her caravan. The capacitor has a capacitance of  $90.0\text{ F}$ , and is fully charged by connecting it to a  $4.20\text{ V}$  battery. Mereana discharges the capacitor for  $2500\text{ s}$  through a  $6.00\ \Omega$  resistor to model the caravan circuit.




- (i) Sketch a graph of current against time for  $2500\text{ s}$  after the switch is closed.

Your graph should include the initial current and the final current after one time constant.

Show all calculations clearly.

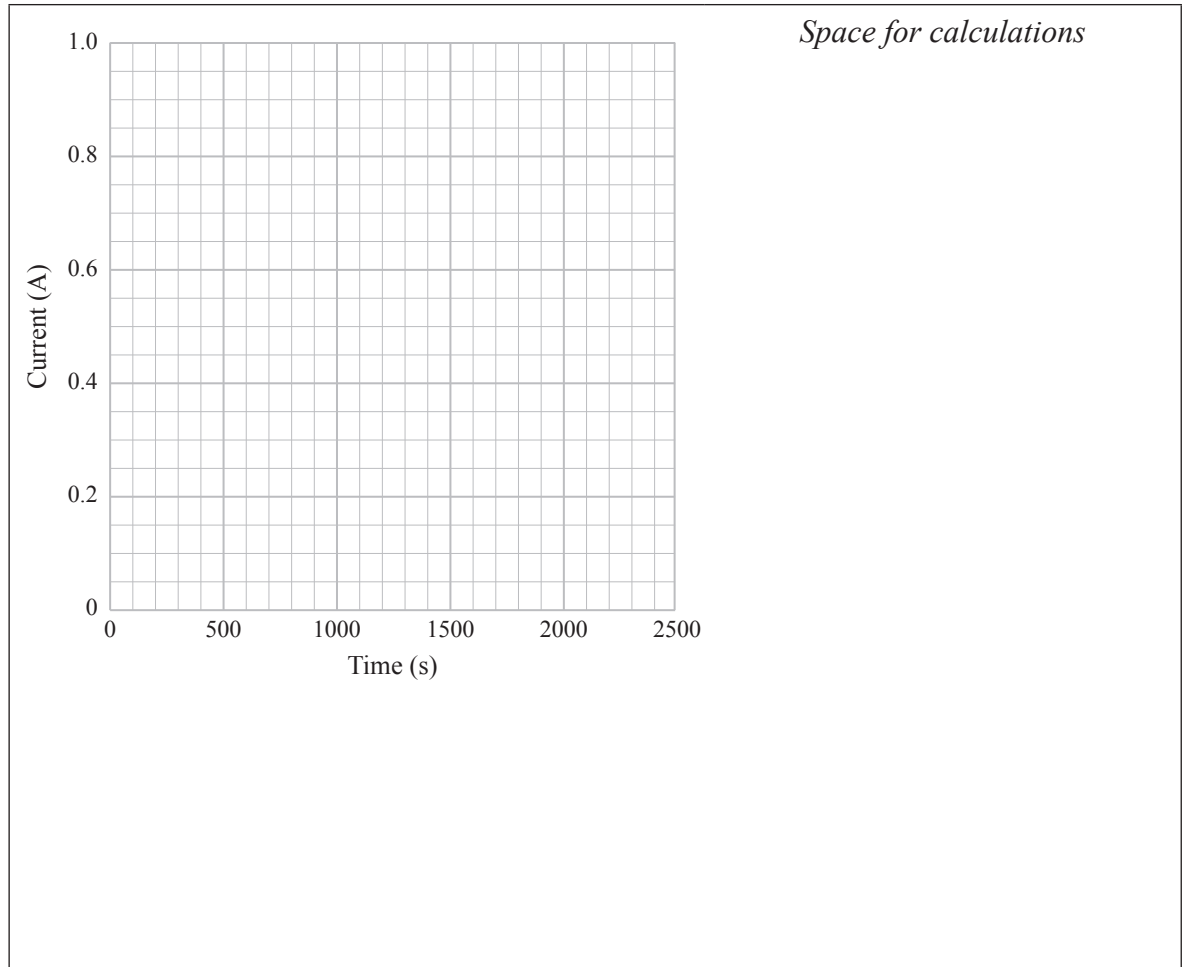*If you need to redraw your response, use the diagram on page 10.*



- (ii) Explain, using physics principles, why the graph has the shape you have drawn.

---

---

---

---

---

---

---

---

---

---




### Circuit B

*You may use calculations to support your answer.*
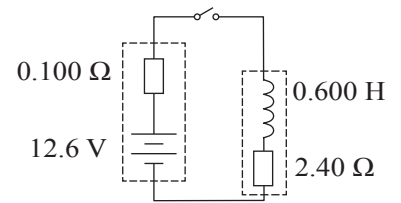
## QUESTION TWO: INDUCTORS

Mereana finds an old coil and connects it to her caravan battery. The corresponding circuit diagram is shown. The coil can be modelled as an inductor with an inductance of  $0.600 \text{ H}$ , and a resistor with a resistance of  $2.40 \Omega$ .




- (a) State the size of the induced EMF across the inductor when the switch is first closed.
- (b) Calculate the size of the induced EMF across the inductor  $0.240 \text{ s}$  after the switch is closed.

- (c) When the switch is opened, a small spark is observed where the switch breaks the circuit. Explain why the small spark is produced.

- Calculate the capacitance required to store this energy when the capacitor is fully charged by the 12.6 V battery.
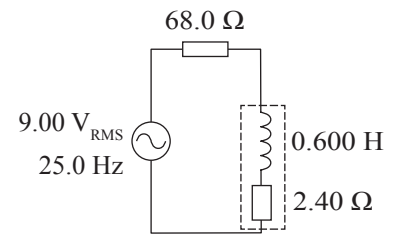
### QUESTION THREE: AC INDUCTORS AND CAPACITORS

Mereana takes the coil back to school, and connects it to a variable frequency AC supply. The  $0.600\text{ H}$  coil (modelled as an ideal inductor and a resistor) is now connected in series with a  $68.0\ \Omega$  resistor to the supply, set to  $25.0\text{ Hz}$  and  $9.00\text{ V}_{\text{RMS}}$  as shown.



- (a) Show that the reactance of the inductor is  $94.2\ \Omega$ .

---



---

- (b) Mereana notices that she can insert an iron nail inside the coil.

Explain what effect this would have on the RMS voltage across the  $68.0\ \Omega$  resistor.

---



---



---



---



---



---



---



---

- 
- 9.00 V<sub>RMS</sub>  
25.0 Hz
- 68.0 Ω
- 0.600 H  
2.40 Ω
- $1.20 \times 10^{-4}$  F


*No calculations are required.*



- (d) The supply frequency of the circuit in part (c) is then further reduced.

Calculate the RMS current in the circuit when the frequency of the supply is 16.0 Hz.


*A phasor diagram may assist your answer.*




*If you need to redraw  
your response, use the  
box on page 10.*

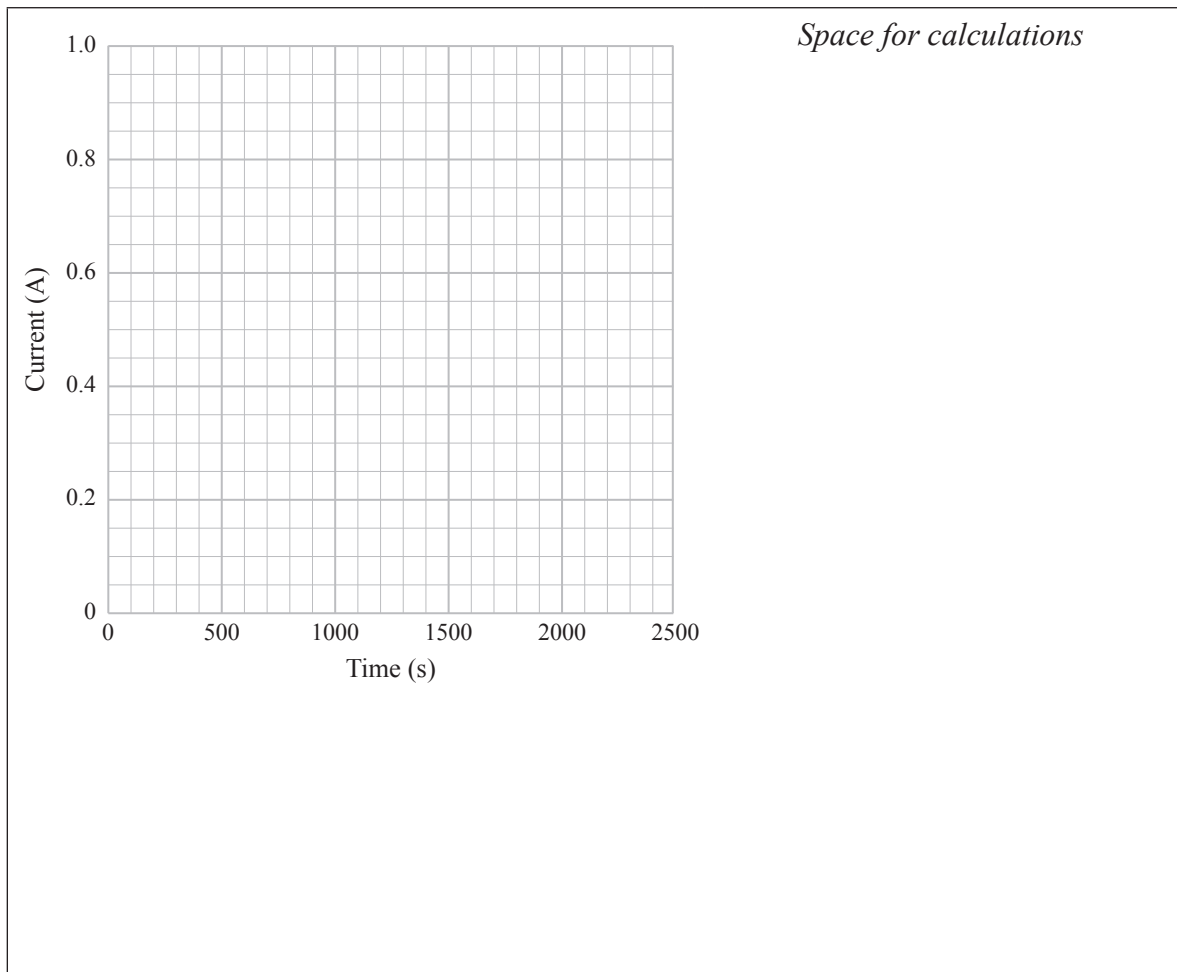**SPARE DIAGRAMS**

If you need to redraw your response to Question One (c), use the diagram below. Make sure it is clear which answer you want marked.



 If you need to redraw your response to Question Three (d), use the box below. Make sure it is clear which answer you want marked.



Extra space if required.  
Write the question number(s) if applicable.

[illegible]

Extra space if required.  
Write the question number(s) if applicable.

QUESTION  
NUMBER

91526